

Analog Lab
Midsem solutions & Marking Scheme
Total 25 marks

1. Testing of the IC TL071 (2 marks)

give +1 mark each of both of the IC's successfully tested.

$$V_{out} = V_{in}$$

2. Triangular Wave generator.

1. First Part: Analysis of Circuit


(a) Analysis of Subcircuit 1 (6 Marks)


1) Positive Feedback (0.5 mark)

2) if Schmitt trigger \rightarrow 0.5 Marks
if Non-inverting Schmitt trigger \rightarrow 1 mark } 1 Marks

3) Virtual ground \rightarrow Not applicable (0.5 Marks)

4) Derivation

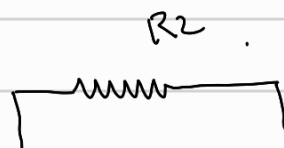

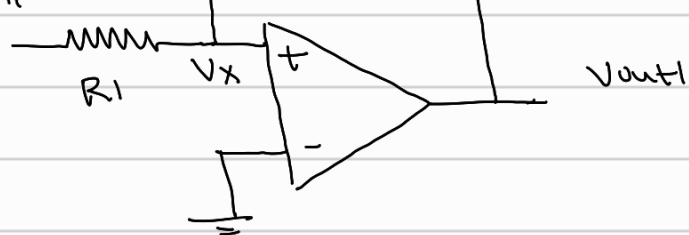

Using KCL

$$\frac{V_x - V_{in1}}{R_1} + \frac{V_x - V_{out}}{R_2} = 0$$

When $V_x = 0$ the V_{out} would change.

@ $V_x = 0$

$$V_{in1} = \frac{R_1}{R_2} (-V_{out})$$

LTP

$$V_{in1} = -\frac{R_1}{R_2} V_{SAT} \quad \left. \vphantom{\frac{R_1}{R_2}} \right\} 0.5M$$

UTP

$$V_{in} = \frac{R_1}{R_2} V_{SAT} \quad \left. \vphantom{\frac{R_1}{R_2}} \right\} 0.5M,$$

- 5) **+1** marks for making the circuit
+1 marks for plotting V_{in} & V_{out} simultaneously on DSO
+1 marks for verifying the theoretical expression with experiment $(\pm 0.3V)$

$$V_{UTP} = \frac{R_1}{R_2} \times 15 = \frac{15}{2.2} = 6.818$$


$$V_{LTP} = \frac{-15}{2.2} = -6.818$$

b) Analysis 1 Subcircuit 2 (5 Marks)

i. Negative Feedback (0.5 Marks)

ii. Integrator circuit (1 Mark)

iii. Yes (0.5 Marks)

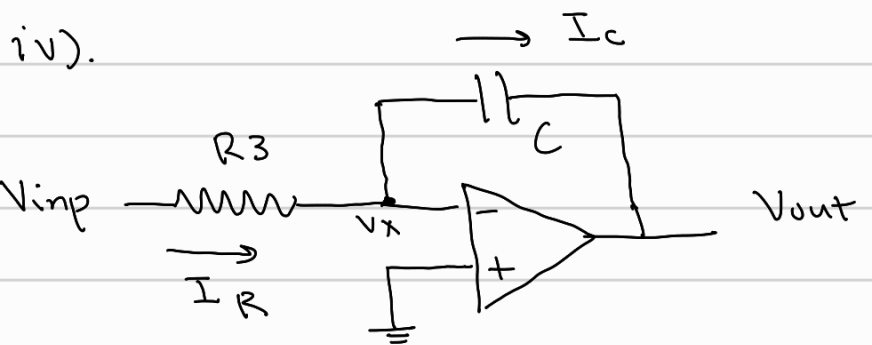

$$I_R - I_C = 0 \quad (KCL)$$

$$q = CV$$

$$I_C = C \frac{dV}{dt} = C \frac{d(V_x - V_{out})}{dt} = -C \frac{dV_{out}}{dt} \quad \left\{ \because V_x = 0 \right\}$$

$$I_C = -C \frac{dV_{out}}{dt}$$

$$I_R = \frac{V_{in} - V_x}{R_3} = \frac{V_{in}}{R_3}$$

$$I_R - I_C = 0$$

$$\frac{V_{in}}{R_3} + C \frac{dV_{out}}{dt} = 0$$


$$V_{out} = -\frac{1}{R_2 C} \int V_{in} \cdot dt$$

+1 for I_R

+1 for I_C

+1 for V_{out} vs V_{in}

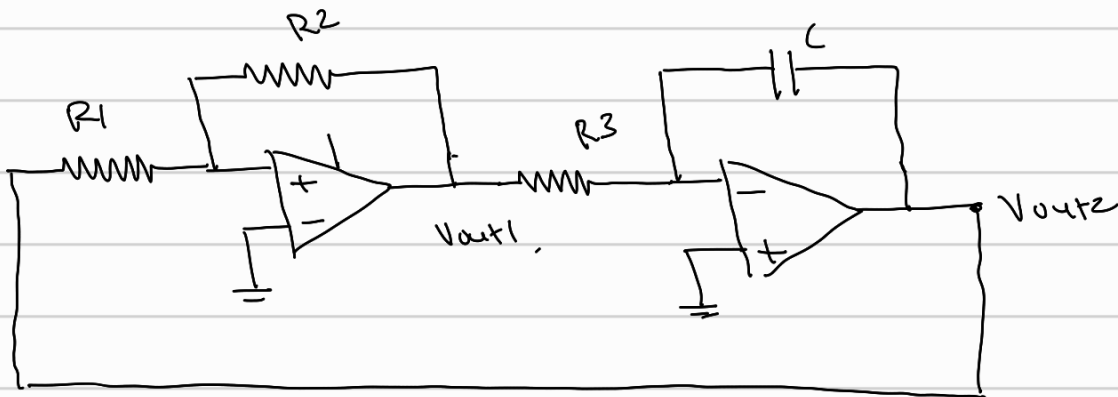c) Analysis of Integrated Circuit (6 marks)




initial condition

$$V_{out1} = +V_{SAT}$$

$$V_{out2} = V_{UTP}$$

$$V_{C1} = V_{UTP}$$

(i)

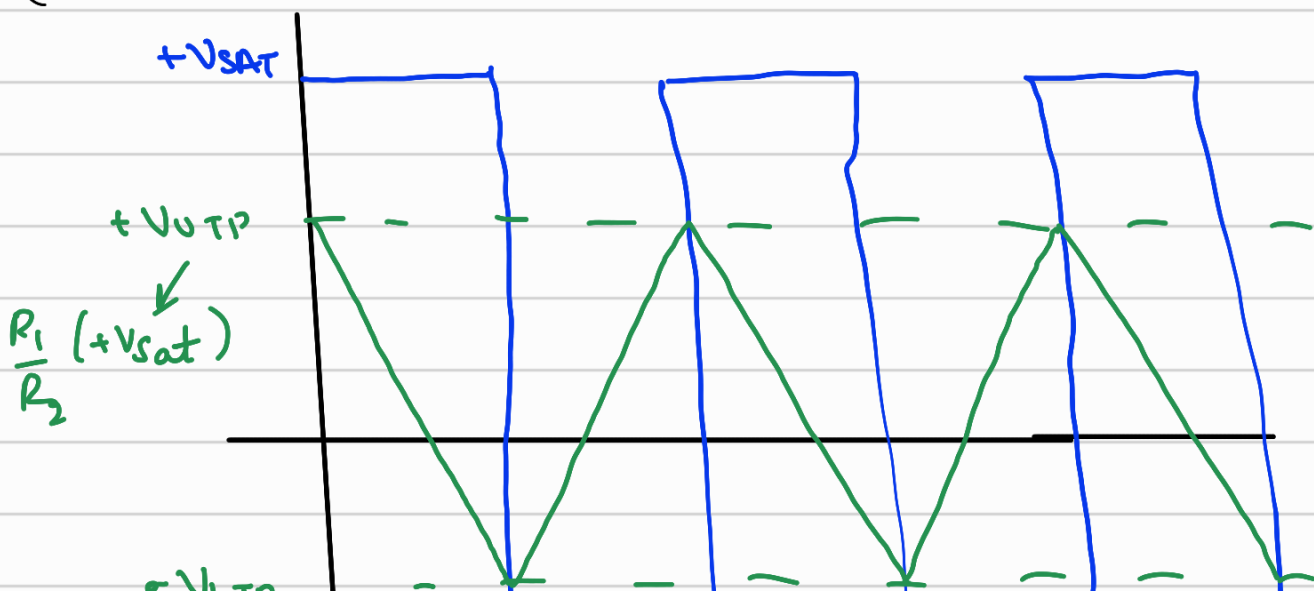

$$\frac{R_1}{R_2} (-V_{sat})$$

$-V_{SAT}$

+1 for drawing triangular wave
+1 for drawing square wave

(ii) Assuming initial condition, & also the fact that when non-inverting terminal voltage of First Op-Amp reaches zero we switch from $V_{SAT} \rightarrow -V_{SAT}$ we get.


$$V_{UTP} = \frac{R_1}{R_2} V_{SAT}$$

$$V_{LTP} = -\frac{R_1}{R_2} V_{SAT}$$

$$V_{pp} = \frac{2R_1}{R_2} V_{SAT}$$

(+1 for getting peak to peak)

Also, assuming initial conditions.

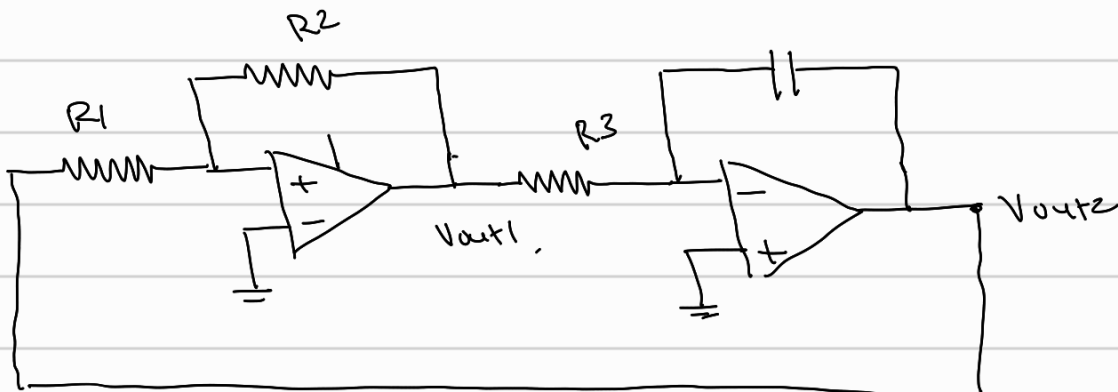

$$V_{out1} = +V_{SAT}$$

$$V_{out2} = -\frac{1}{R_3 C} \int_0^t V_{out1} \cdot dt.$$

from 0 to $T/2$ the output swings from.

$$V_{uTP} \rightarrow V_{LTP}.$$

$$V_{out2} = -\frac{1}{R_3 C} \int_0^{T/2} V_{SAT} \cdot dt.$$

$$V_{pp} = -\frac{1}{R_3 C} \int_0^{T/2} V_{SAT} \cdot dt.$$

$$\frac{2R_1}{R_2} V_{SAT} = -\frac{1}{R_3 C} V_{SAT} \frac{T}{2}$$

$$T = \frac{4 R_1 C R_3}{R_2}$$

$$f = \frac{R_2}{4 R_1 R_3 C}$$

+3 for getting expression of frequency

2. Determining the Component Values (2 marks)

(a) $V_{pp} = 20$ +1 for getting Amp value.

$$2R_1 V_{SAT} = 20$$

$$\frac{R_1}{R_2} = \frac{10}{15} = \frac{2}{3}$$

$$\frac{R_1}{R_2} = \frac{2}{3} \quad \text{e.g. } R_2 = 1k$$

$$R_1 = \frac{2}{3} \times 1 = 667 \Omega$$

(b) $f = 2.5kHz$

$$2.5k = \frac{R_2}{4R_1R_3C}$$

$$R_3 = \frac{R_2}{4R_1 \times 2.5 \times 10^3 \times 100 \times 10^{-9}}$$

$$R_3 = \frac{3}{4 \times 2 \times 2.5 \times 10^3 \times 100 \times 10^{-9}}$$

$$R_3 = \frac{3}{10 \times 10^3 \times 100 \times 10^{-9} \times 2}$$

$$R_3 = \frac{1.5}{10^6 \times 10^{-9}}$$

$$R_3 = \frac{1.5}{10^{-3}}$$

$$R_3 = 1.5k$$

$$C = 0.1 \mu F$$

+1 for getting appropriate values of R_2 & C

+1 for getting appropriate ratio from K_1 & K_2

* STUDENTS MAY USE DIFFERENT COMBINATIONS *

3. Hardware Implementation. (4 marks)

+1 for correct peak to peak values of square wave

+1 for correct frequency of square wave

+1 for correct peak to peak value of triangular wave

+1 for correct frequency of triangular wave

$$f_{\text{req TOL}} = \pm 100 \text{ Hz}$$

$$\text{Amp} = \pm 0.1 \text{ V}$$