

Solution : Assignment 1

(Q-1) :- \Rightarrow old configuration :-

Train has 8 coaches + 1 locomotive.

\downarrow 30 wheels. (All Dummy)	\downarrow 30 wheels out of which 20 Driving wheels. 10 Dummy wheels.
---	--

Traction Force developed by the locomotive is

$$F_{T_{Loco}} = \mu \left(\frac{w}{30} \right) * 20 = \frac{2}{3} w \mu \quad \text{--- (2)}$$

where 'w' is the weight of locomotive = weight of coach
= weight of motorized coach.

\Rightarrow New configuration :- Suburban Train (EMU)
of 8 coaches. --- (1)

Given $F_{T_{EMU}} = 4 * F_{T_{Loco}} = 4 * \frac{2}{3} w \mu = \frac{8}{3} w \mu$

The no of Driving wheels required to generate this force.

are = $\frac{\left(\frac{8}{3} w \right) \mu}{\left(\frac{w}{30} \right) \mu} = 80 \quad \text{--- (2)}$

Total no of wheels in all the 8 coaches (EMU)

$$= 30 \times 8 = 240.$$

out of which

80 are
Driving wheels

160
Dummy wheels

--- (1)

Configuration - 1 :-

Assuming all 8 coaches are motorized coaches.
each coach having 10 driving wheels $\rightarrow 8 \times 10 = 80$
20 Dummy wheels $\rightarrow 8 \times 20 = 160$
240.

$$F_{\text{TEMU}(1)} = 8 * \frac{\omega}{30} * 10 * C_m = \frac{8}{3} \omega * C_m \quad (4)$$

Configuration - 2 :-

Assuming 4 motorized coaches and
4 trailer coaches.

each having	<u>4 motorized coaches</u>	<u>4 trailer coaches.</u>
20 Driving wheels	$\rightarrow 4 \times 20 = 80$	No Driving wheels
10 Dummy wheels	$\rightarrow 4 \times 10 = 40$	30 Dummy wheels
	<u>120</u>	$\rightarrow 4 \times 30$
		<u>= 120</u>

$$F_{\text{TEMU}(2)} = 4 * \frac{\omega}{30} * 20 * C_m$$

$$= \frac{8}{3} \omega * C_m$$


(240)

*


2 When S is on:


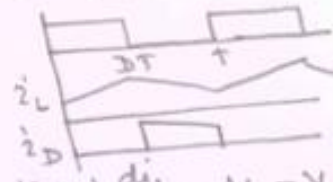
$$V_L = L \frac{di_L}{dt} = V_d - r i_L$$


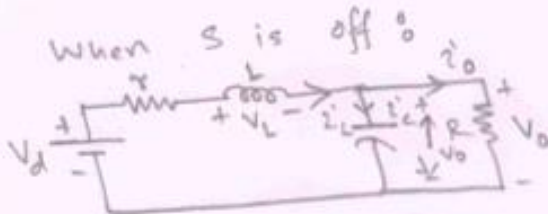
$$V_L = L \frac{di_L}{dt} = V_d - V_o - r i_L$$



At steady state average voltage drop across the inductor is zero

$$\therefore (V_d - r i_L)DT + (V_d - V_o - r i_L)(1-D)T = 0$$

$$\text{or, } V_o(D-1) = r i_L - V_d \quad \left| \begin{array}{l} \therefore I_o = (1-D) \bar{i}_L \\ \therefore \bar{i}_L = \frac{I_o}{1-D} \end{array} \right.$$

$$\approx r \bar{i}_L - V_d = r \frac{I_o}{(1-D)} - V_d = \frac{r}{R} \frac{V_o}{1-D} - V_d$$

$$\text{or, } V_o(1-D) = V_d - \frac{r}{R} \frac{V_o}{1-D} \quad \text{or } V_o = \frac{V_d(1-D)}{\frac{r}{R} + (1-D)^2}$$


$$\therefore \text{At } D=0, V_o = \frac{V_d}{\frac{r}{R} + 1} \times R \approx V_d \text{ (if } r \text{ is small)}$$

At $D=1$, $V_o=0$, Hence $V_o(\max)$ occurs in the range of $0 \leq D \leq 1$

$$\frac{dV_o}{dD} = 0 \Rightarrow -\left\{ \frac{r}{R} + (1-D)^2 \right\} V_d - V_d(1-D)(2D-2) = 0$$

$$\text{or, } D = 1 - \sqrt{\frac{r}{R}}$$
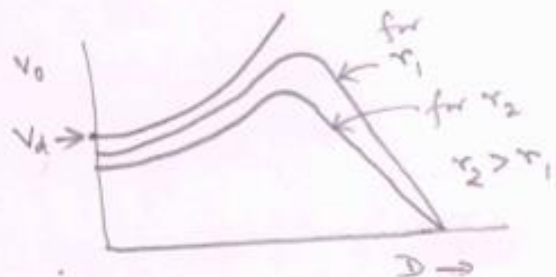
$$\therefore V_o(\max) = \frac{V_d}{2} \sqrt{\frac{R}{r}}$$




3. i) $T = 5 \times 10^{-5} \text{ s}$

$$I_{up} = \frac{100}{L} DT$$

and

$$I_{up} - \frac{400}{L} (1-D)T = 0$$
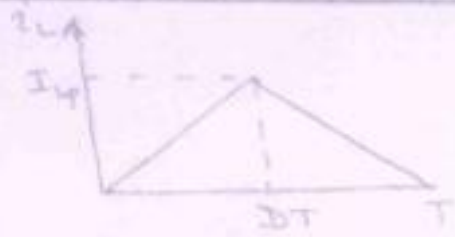
$$\therefore \frac{100}{L} DT - \frac{400}{L} (1-D)T = 0 \quad \therefore D = 0.8$$



ii) As $D = 0.5$ which is less than 0.5, the system operates in discontinuous mode of operation

$$\text{Power transferred} = \frac{\text{Energy stored in the inductor at } DT}{T}$$

$$I_{up} = \frac{100}{L} DT$$

$$= \frac{100}{100 \times 10^{-6}} \times 0.5 \times 5 \times 10^{-5}$$

$$= 25 \text{ A}$$




$$\therefore \text{Energy stored in the inductor at } DT = \frac{1}{2} \times L \times (25)^2 \text{ W}$$

$$\therefore \text{Power transferred} = \frac{1}{2} \times 100 \times 10^{-6} \times 625 \times \frac{1}{5 \times 10^{-5}} \text{ W}$$

$$= 625 \text{ Watt}$$

iii) Inductor current will continually build up and steady state will never be reached.

94

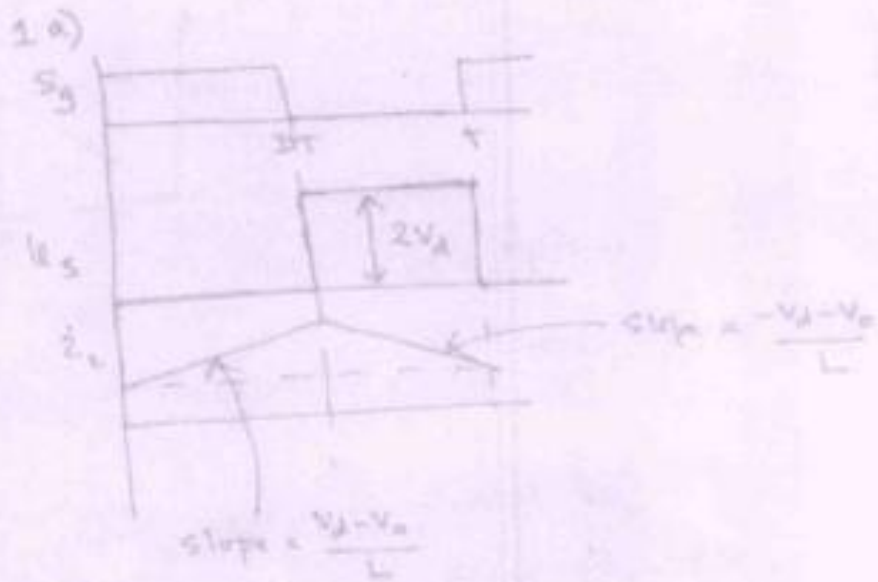

2) Average voltage across the inductor is zero.

$$\therefore (V_d - V_o)DT - (V_o + V_o)(1-D)T = 0$$

$$\therefore V_o = (2D-1)V_d.$$

$$I_{rr} = \frac{V_d - V_o}{L} DT = 2V_d(1-D)\frac{DT}{L}$$


Q5

As the converter is on the boundary of continuous and discontinuous mode of conduction

$$L = 50 \times 10^{-6} \text{ H}$$

$$T = \frac{1}{50 \times 10^3} \text{ s}$$

$$= 2 \times 10^{-5} \text{ s}$$

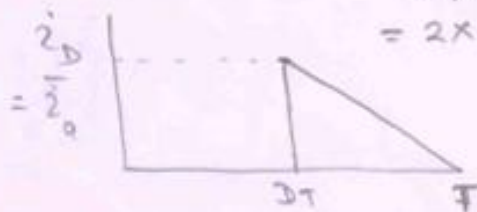

$$\frac{V_o}{V_d} = \frac{D}{1-D}$$

$$\text{or, } V_d = \frac{1-D}{D} V_o$$

$$I_{D(\text{peak})} = \frac{V_d}{L} DT \quad \therefore \bar{i}_D = I_0 = \frac{1}{2} (1-D)T \times \frac{V_d}{L} DT \times \frac{1}{T}$$

$$= \frac{10}{R_L}$$

$$\frac{D(1-D)T}{100 \times 10^{-6}} \times V_d = \frac{10}{R_L}$$

$$\frac{D(1-D)T}{100 \times 10^{-6}} \times \frac{1-D}{D} V_o = \frac{10}{R_L}$$

$$\text{or } \frac{(1-D) \times 2 \times 10^{-5}}{100 \times 10^{-6}} \times \frac{1-D}{D} V_o = \frac{10}{R_L}$$

$$\text{or } (1-D)^2 = \frac{5}{R_L} \quad \text{or, } 1-D = \pm \sqrt{\frac{5}{R_L}} \quad \text{or } D = 1 \pm \sqrt{\frac{5}{R_L}}$$

D cannot be more than 1.

$$\therefore D = 1 - \sqrt{\frac{5}{R_L}}, \quad V_d = \frac{1 - 1 + \sqrt{\frac{5}{R_L}}}{1 - \sqrt{\frac{5}{R_L}}} \times 10 = \frac{\sqrt{\frac{5}{R_L}}}{1 - \sqrt{\frac{5}{R_L}}} \times 10 \text{ V}$$

$$I_{D(\text{peak})} = \frac{V_d}{50 \times 10^{-6}} (1 - \sqrt{\frac{5}{R_L}}) \times 2 \times 10^{-5} \text{ A}$$

$$= \frac{2V_d}{5} (1 - \sqrt{\frac{5}{R_L}})$$

$$= \frac{2}{5} \frac{\sqrt{\frac{5}{R_L}}}{1 - \sqrt{\frac{5}{R_L}}} (1 - \sqrt{\frac{5}{R_L}}) \times 10 \text{ A}$$

$$= 10 \times \frac{2}{5} \sqrt{\frac{5}{R_L}} \text{ A} = \frac{20}{\sqrt{5R_L}} \text{ A}$$


Q6 $\delta = 0.5$, therefore the o/p. voltage should have been 50V, if the converter operates under continuous mode of conduction.

As $V_o = 80 > 50V$, the converter is operating under discontinuous mode of conduction.

$$I_{Lp} = \frac{20}{2.5 \times 10^{-3}} T \times 0.5 \cdot S_g$$

$$T = \frac{1}{5 \times 10^3}$$

$$= 2 \times 10^{-4}$$

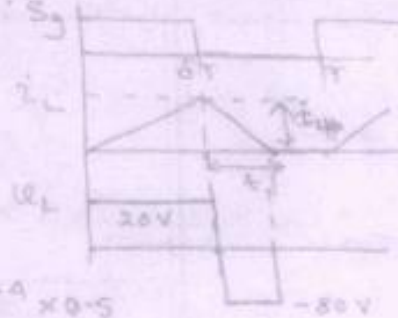

$$\therefore I_{Lp} = \frac{20}{2.5 \times 10^{-3}} \times 2 \times 10^{-4} \times 0.5$$

$$= 0.8A$$

Average voltage drop across the inductor is 2V.

$$\therefore 20 \times 1 \times 10^{-4} - 80 t_1 = 0$$

$$\therefore t_1 = \frac{20 \times 10^{-4}}{80} = 0.25 \times 10^{-4}$$

$$\therefore \bar{i}_L = I_o = \frac{1}{2} \times (1.25 \times 10^{-4}) \times 0.8 \times \frac{1}{2 \times 10^{-4}}$$

$$= 0.25A$$

$$\therefore R_L = \frac{80}{0.25} A = 320 \Omega$$