

Mid Sem - 2024  
EE-238, Solution.

Q1. In continuous mode of conduction.

$$V_o = \frac{\delta}{1-\delta} V_d \quad \text{or} \quad \frac{150}{100} = \frac{\delta}{1-\delta} \quad \text{or} \quad \delta = 0.6$$

The o/p current below which the converter enters into discontinuous mode of conduction at  $\delta = 0.6$  is

$$I_{OB} = \frac{V_d T}{2L} \delta(1-\delta) \quad V_d = 100, \quad T = \frac{1}{5 \times 10^3} = 0.2 \times 10^{-3} \text{ s}$$
$$= \frac{100 \times 0.2 \times 10^{-3}}{2 \times 2.5 \times 10^{-3}} \times 0.6 \times 0.4 \text{ A} = 0.96 \text{ A}.$$

The o/p current of the converter is  $\frac{150}{500} \text{ A} = 0.3 \text{ A}.$

As  $0.3 \text{ A} < 0.96 \text{ A} \Rightarrow$  the converter is operating in disc. mode and  $\delta \neq 0.6$ . — (2 marks)  
~~0.6 is considered~~

$$\therefore \frac{V_o}{V_d} = \frac{V_d T}{2L} \times \frac{\delta^2}{I_o} = 4 \times \frac{\delta^2}{0.3} = \frac{150}{100}$$

$$\text{or } \delta^2 = \frac{150 \times 0.3}{400} = 0.1125$$


$$\text{or } \delta = 0.335 \quad (\text{discarding } \text{neglecting} \text{ the -ve value.})$$

While testing continuous mode or discontinuous mode of operation if  $\delta$  is considered to be 0.5, and  $I_{OB}$  is ~~for~~ considered to be

$$\frac{V_d T}{8L} = \frac{100 \times 0.2 \times 10^{-3}}{8 \times 2.5 \times 10^{-3}} = 1 \text{ A} \quad (\text{deduct 1 mark.})$$

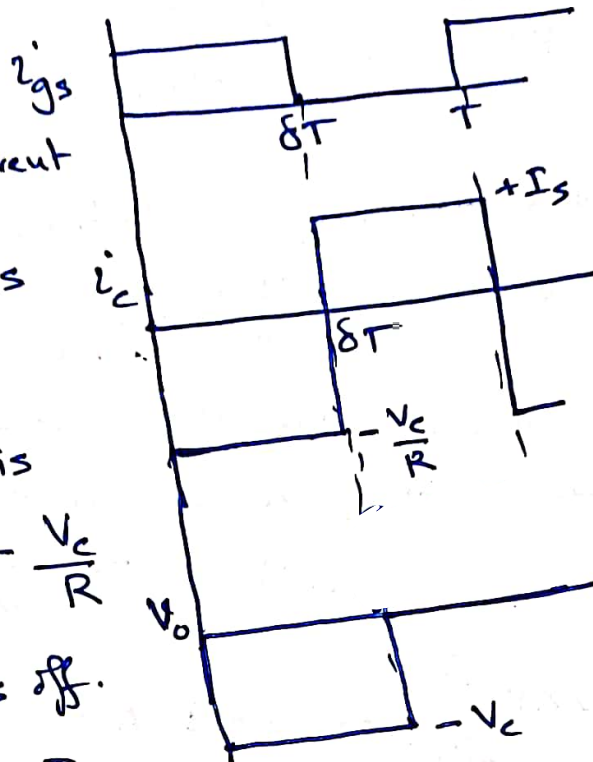Q2.

Let the current through the capacitor is  $i_c$



2 marks


When S is on,  $i_c = -\frac{V_c}{R}$

2 marks

When S is off,

$$i_c = +I_s$$

When S is on,  $V_o = -V_c$

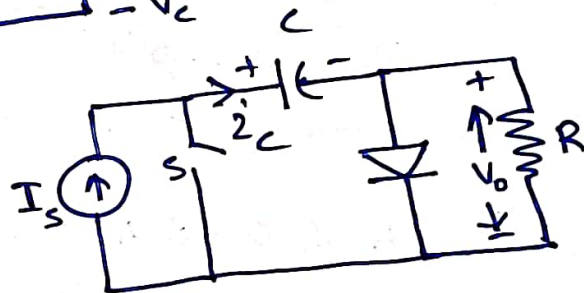

2 marks

When S is off,  $V_o = 0$  as the diode is conducting.

Average current through C is zero at steady state

$$\therefore -\frac{V_c}{R} \delta T + I_s (1-\delta) T = 0$$

2 marks

$$\text{or, } V_c = \frac{R I_s (1-\delta)}{\delta}$$


ii)

$$V_o = -V_c \delta T / T = -V_c \delta = -R I_s (1-\delta)$$


2 marks

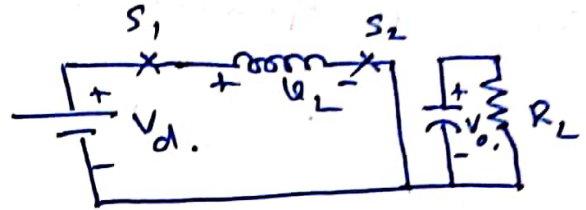Q3. When  $S_1$  and  $S_2$  are on :


the equivalent ckt :  
The voltage across the inductor,  $V_L = +V_d$ .



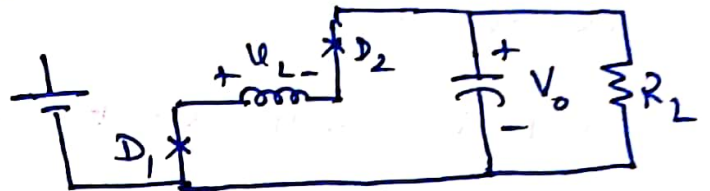2 marks When  $S_1$  and  $S_2$  are off,  $D_1$  and  $D_2$  conduct, and the voltage across the inductor,  $V_L = -V_o$ .



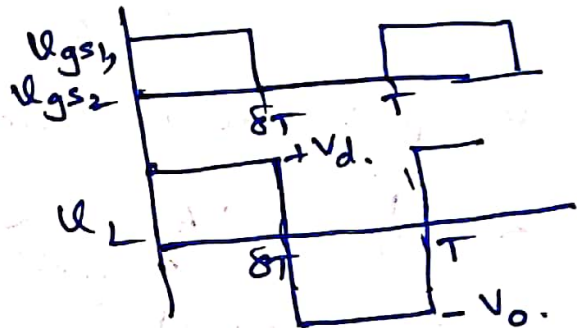Average voltage drop across any inductor is zero



$$\therefore V_d \delta T - V_o (1 - \delta) T = 0$$

$$\therefore \frac{V_o}{V_d} = \frac{\delta}{1 - \delta}$$

2 marks

the circuit is functioning as a  
buck-boost converter — 0.5 marks  
in non-inverting mode — 0.5 mark

Q4

Let us assume that the flyback converter is operating in continuous mode of operation

$$\therefore V_o = \frac{N_2}{N_1} \cdot \frac{\delta}{1-\delta} \cdot 100 = \frac{1}{2} \cdot \frac{0.25}{0.75} \times 100 = 16 \text{ V}$$

the o/p voltage is 80V, hence it is operating in disc. mode.

The peak switch current = peak magnetizing current


$$= I_{Lp} = \frac{100 \times 0.25 \times 20 \times 10^{-6}}{250 \times 10^{-6}} = 2 \text{ A} \quad (2 \text{ marks})$$

Now, the peak diode current

$$= 2 \times \frac{N_1}{N_2} = 4 \text{ A} \quad (2 \text{ marks})$$

Average diode current
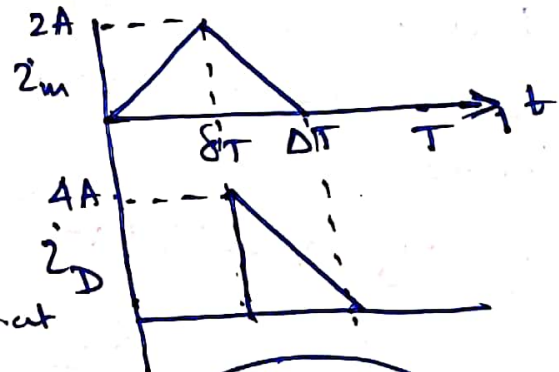
$$= \frac{1}{2} \times 4 \times \Delta T \times \frac{1}{T} = \text{Average } I_D \quad \text{Low current}$$



$$\text{or } 2 \text{ A} = \frac{80}{R_L} \quad \text{or } \Delta = \frac{40}{R_L} \quad \text{--- (1)} \quad (3 \text{ marks})$$


$\therefore$  Average voltage drop across the magnetizing inductance is zero

$$100 \delta T - 160 \Delta T = 0$$

$$\text{or } \Delta = \frac{100}{160} \times 0.25 = 0.156$$

$$\text{By (1)} \quad \frac{40}{R_L} = 0.156$$

$$\therefore R_L = 256.41 \Omega$$

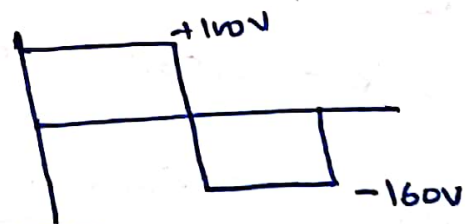

(3 marks)



Q5 A)



1 mark


If  $T/2$  and  $T$  are not marked deduct  $1/2$  mark.

1 mark.


1 mark.

2 marks.

Q5

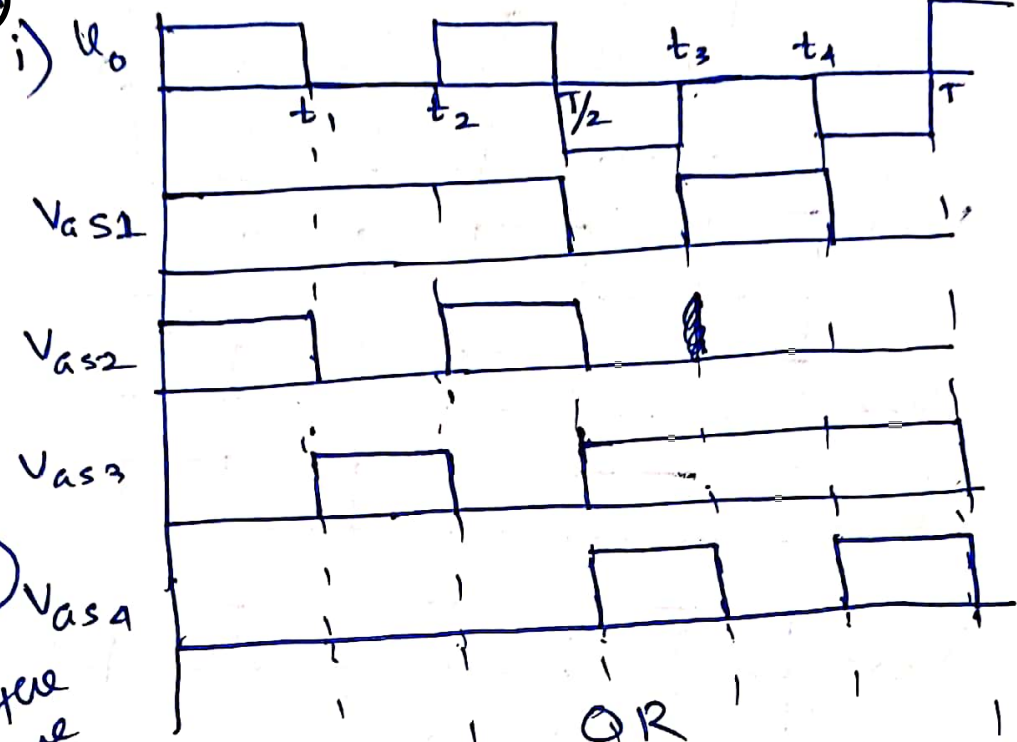


OR

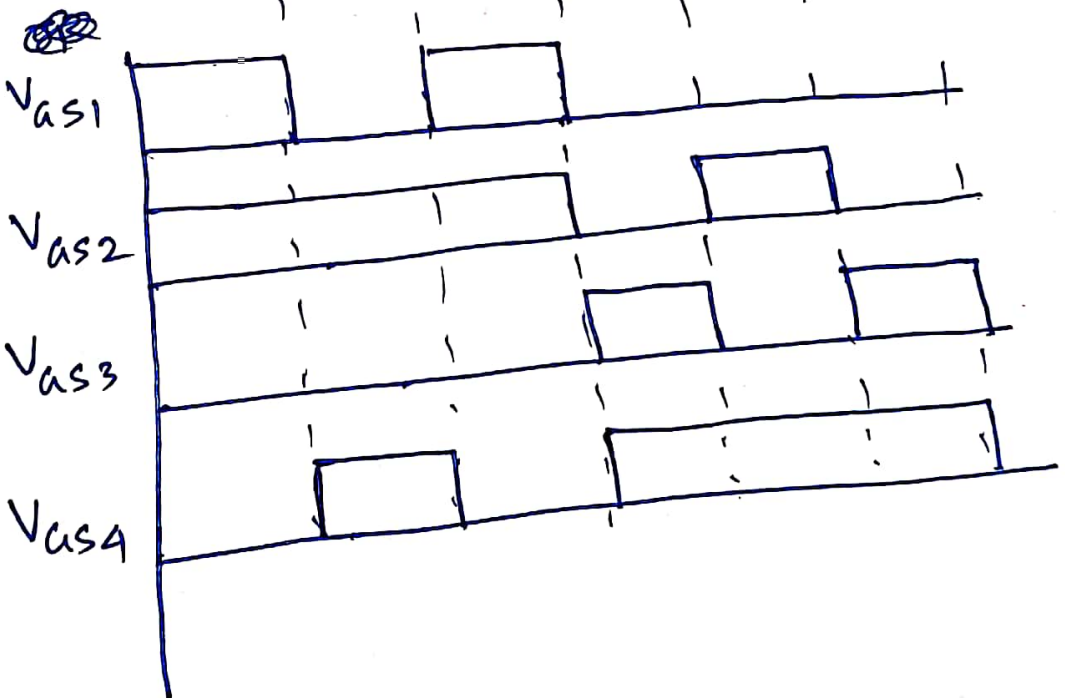

3 marks if any one of the options are provided. If all the switches are kept open during the 'zero' instant of  $v_o$ , no credit to be given.


Q5 B

ii)

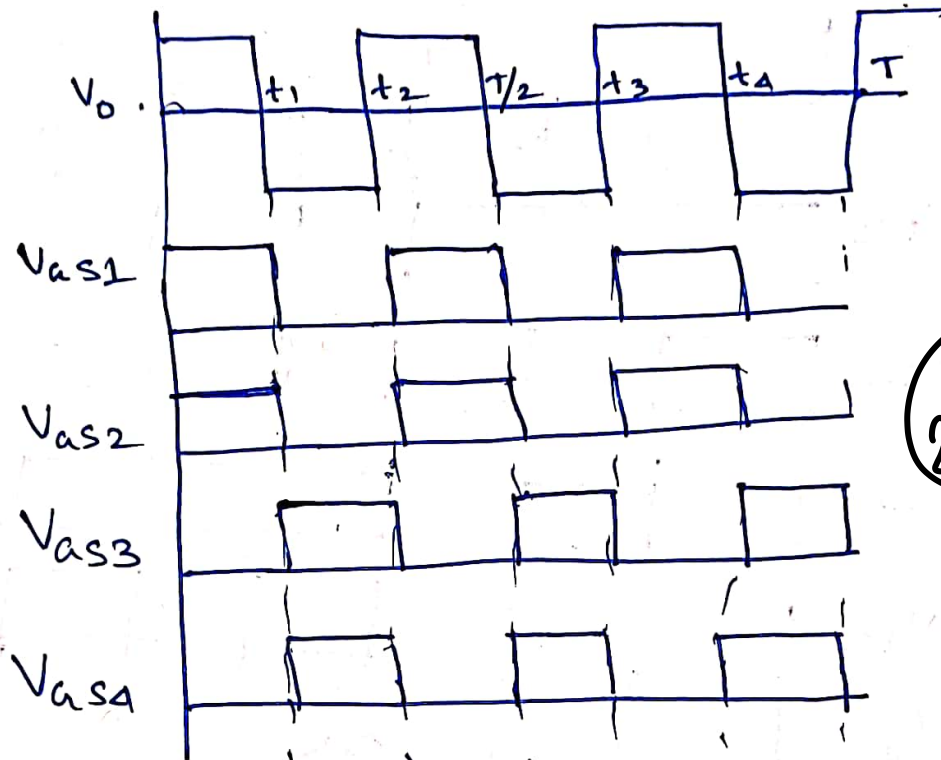

2 marks

Q6 a)

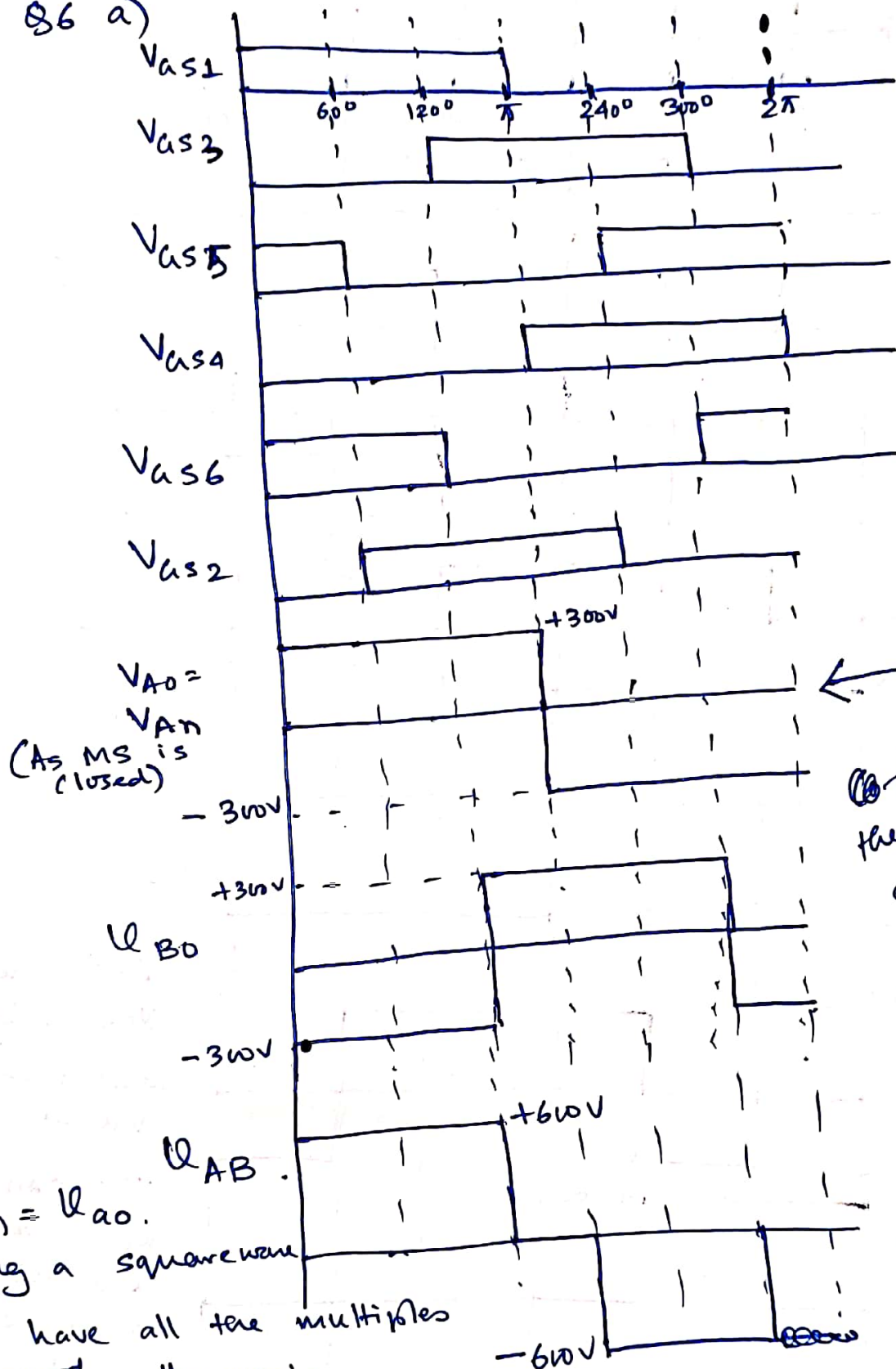

1 mark.

for correctness of the rest of the diagram 1 mark.

$$U_{AN} = U_{AO}$$

being a square wave

will have all the multiples of 3rd Harmonic

$$U_{AB} = U_{AO} - U_{BO}$$

the third harmonics ~~are~~ will get cancelled as the  $U_{AO}$  and  $U_{BO}$  are displaced from each other by  $120^\circ$ .

1 mark.



Q6 B)

$V_{as1}$

$V_{gs3}$

$V_{gs5}$

$V_{gs4}$

$V_{gs6}$

$V_{gs2}$

+300V

$V_{Ao}$

-300V

+300V

$V_{Bo}$

300V

+600V

$V_{AB}$

300V

-600V

5 marks if justification is provided

150V

150V

-150V

Both line to line voltage, i.e.  $V_{AB}$  and phase to neutral voltage i.e.  $V_{Ao}$  do not have any third harmonic component.

1 mark


-300V

1) 0 to 60°

$$I = \frac{600}{\frac{20}{3} + 20} \text{ A}$$

$$= \frac{600}{\frac{80}{3}} = \frac{15 \times 600 \times 3}{80}$$

$$= 15 \times \frac{3}{2} \text{ A.}$$

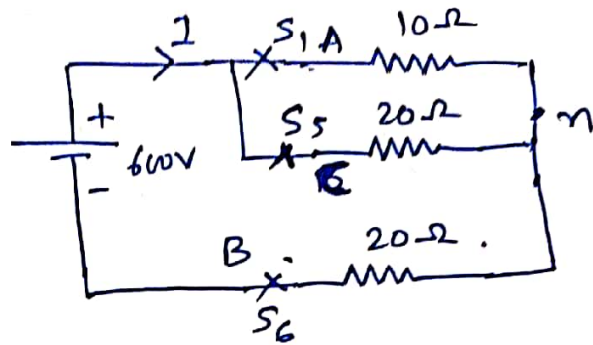

∴ Voltage drop  $V_{nB} = 15 \times \frac{3}{2} \times 20 = 450.$


∴ Voltage drop  $V_{An} = V_{cn} = 600 - 450 = \underline{150 \text{ V.}}$

2) 60° to 120°

$$I = \frac{600}{20} \text{ A.}$$


$$\therefore V_{An} = \frac{600}{20} \times 10$$

$$= \underline{300 \text{ V.}}$$

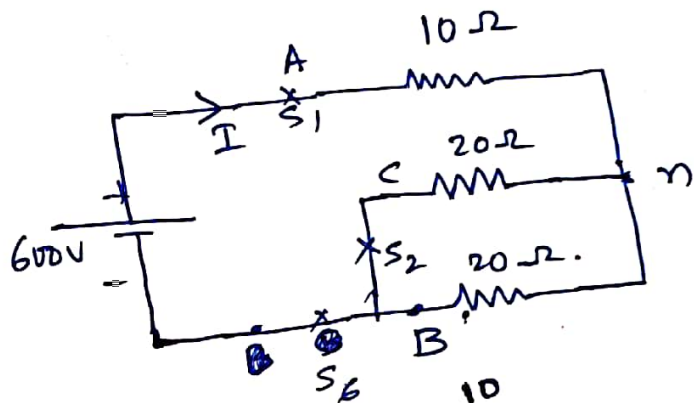

3) 120° to 180°


$V_{An} = 150 \text{ V.}$

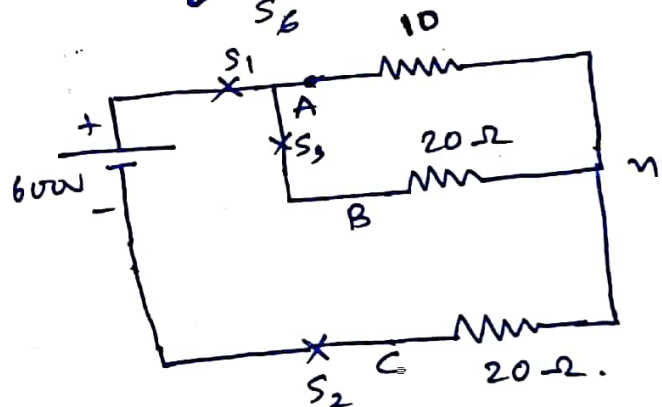

4) 180° to 240°

$$V_{nA} = +150 \text{ V}$$

$$\therefore V_{An} = -150.$$

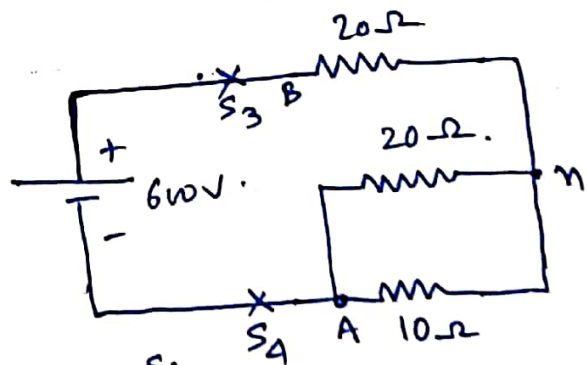

5) 240° to 300°

$$V_{nA} = 300 \text{ V}$$

$$\therefore V_{An} = -300 \text{ V.}$$

