

## Assignment 1

1) A train is having 8 coaches and is driven by a locomotive. The locomotive has 30 wheels out of which 20 are driving wheels. Each coach is having 30 wheels. This train has to be reconfigured as a suburban train having 8 coaches and no locomotive so that it can develop **four times** the maximum tractive effort that can be developed in the locomotive driven train. Further, each coach should have 30 wheels. Assume that the weight of a locomotive, a trailer coach and a motorized coach are equal and is not affected by the weight of the passengers being carried. Further, assume that each driving wheel generates equal tractive effort. Determine the wheel configuration (number of motorized wheels, number of dummy wheels, number of motorized coaches, number of trailer coaches etc.) of the reconfigured train. Once designed do a confirmatory check on it and report its performance regarding its maximum tractive effort.

Q2) Consider the practical boost converter circuit shown in Figure 1 wherein the inductance,  $L$  has a series resistance,  $r$  (which represents the coil resistance of the inductor as well as iron losses of the inductor. Further, it also represents all the losses that are incurred in the circuit). The capacitor,  $C$  is large enough so that the ripple in the output voltage,  $V_0$  of the converter can be neglected. Similarly it can be assumed that the inductor,  $L$  is large enough so that the current ripple in the inductor can be neglected i.e.  $i_L \approx \text{Average of } i_L = I_L$ . The converter is feeding a load having resistance,  $R$ , and it is operating in continuous mode of conduction with a switch duty ratio of  $D$ . A) Determine the relationship,  $\frac{V_0}{V_d}$ . Hence determine  $V_0$  (i)  $D = 0$  and (ii)  $D = 1$ . B) Find the value of  $D$  when  $V_0$  is maximum, and hence determine the maximum value of  $V_0$ .


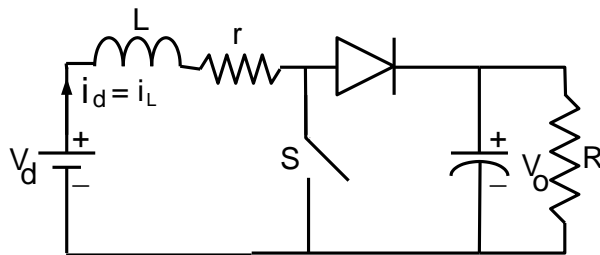
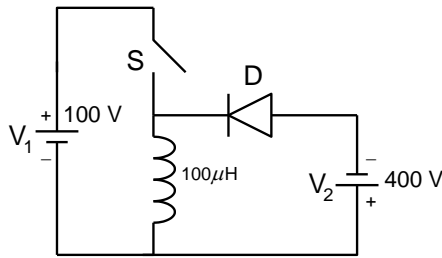


Figure 1

Q3) In Figure 2, the switch is operated at a switching frequency of 20kHz with a duty cycle,  $D$ .  $L = 100\mu\text{H}$ . 1) Find the value of  $D$  at the boundary of continuous and discontinuous mode of conduction. 2) For a value of  $D=0.5$ , find the power transferred from source  $V_1$  to  $V_2$ . 3) Can the circuit operate at steady state under continuous mode of conduction?

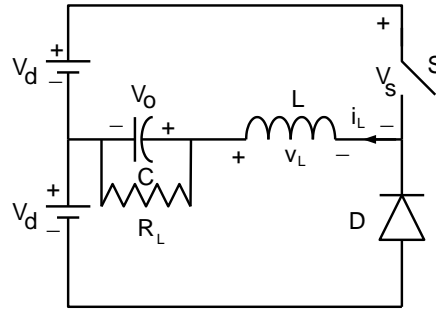

**Figure 2**

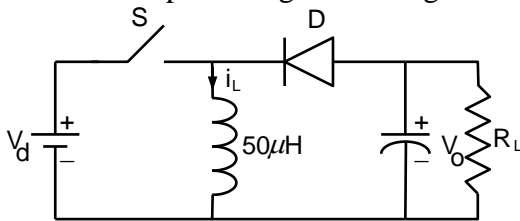


**Figure 3**


Q4) Consider the dc to dc converter circuit shown in Figure 3. The switch is operated with a switching time period,  $T$  and duty cycle,  $D$ .  $V_d$  is the source voltage and  $V_o$  is the output voltage. You may assume that the capacitor is large enough so that ripple in  $V_o$  can be neglected. 1) Draw  $V_s$  and  $i_L$  for a) continuous mode of conduction and b) for discontinuous mode of conduction. 2) For continuous mode of conduction find an expression for  $V_o$  in terms of  $V_d$ ,  $D$  and  $T$ . 3) For continuous mode of conduction find an expression for peak to peak value of  $i_L$  in terms of  $V_d$ ,  $D$ ,  $T$  and  $L$ .

Q5) The buck-boost converter shown in Figure 4 is operated so as to maintain constant output voltage  $V_o = -10V$ , as the input voltage  $V_d$  is varied. The switching frequency is 50kHz. The value of the inductor is 50μH and the value of the capacitor can be assumed to be infinite as compared to other circuit parameters. 1) At the boundary of continuous and discontinuous mode of conduction, what is the value of  $V_d$ . At this boundary what is the magnitude of peak current flowing through the diode.

Q6) For the buck regulator shown in Figure 5, the switch,  $S$  is operated with a duty ratio of 0.5 at a switching frequency of 5kHz. The inductor,  $L$  is having a value of 2.5mH. Input voltage to the regulator is maintained at 100V. The output voltage,  $V_o$  is found to be 80V. Find the value of load resistance  $R_L$  connected to the output of the regulator. Assume the output voltage of the regulator is ripple free.



**Figure 4**

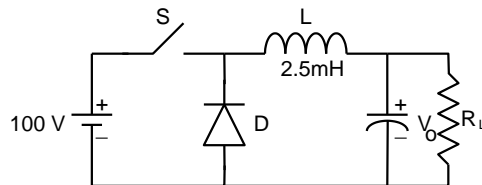

**Figure 5**