 


Roll No.: [22b3936]

Marks: 5.0


Question 1.

For the dc to dc converter shown in the Figure, the switch, S is operated with a switching frequency of 5 kHz. The value of the inductor, L is 2.5 mH. Input voltage, V_d of the converter is maintained at 100 V. The output voltage, V_o is maintained at a value of -150 V while a load resistance, $R_L = 500 \Omega$ is connected to the output terminals of the converter. Determine the duty cycle, δ with which the switch, S is operating. Assume that the output voltage of the regulator is ripple free as the output filter capacitor, C is significantly large.



Rubrics: No rubrics available.

Click to
load preview

 

CHAT

Roll No.: [22b3936]


Marks: 10.0

Question 2.

The input to the dc to dc converter circuit shown in the Figure is a current source having a constant magnitude, I_s , and the converter is feeding a load, R . The switch, S is operated with a period, T and a duty cycle, δ . You can consider that the capacitor, C is large enough, so that the voltage across it can be assumed to be ripple free. Once the circuit has attained steady state of operation determine the following as a function of I_s , δ and R :

 1. Average capacitor voltage, V_C . (7 marks)
2. Average output voltage, V_O . (3 marks)

[Hint: This circuit was not discussed during lecture sessions. Apply the golden rules of steady state circuit analysis, and you will arrive at the expressions asked for]



Rubrics: No rubrics available.



Roll No.: [22b3936]

Marks: 5.0

Question 3.

Consider the converter circuit shown in the Figure - A. The switches S_1 and S_2 are turned on and off simultaneously with the switching, frequency f_s ($=\frac{1}{T}$), and with a duty cycle of d as shown in Figure - B. Assume that the current through the inductor is continuous. 1) Derive the expression of the output voltage, V_o in terms of the given parameters when the circuit is operating at steady state. 2) Comment on the functionality of the circuit. (4+0.5+0.5 marks)

 


Figure A

 


Figure B


Rubrics: No rubrics available.

Roll No.: [22b3936]


Marks: 10.0

 Question 4.

Consider the flyback converter circuit shown in the figure. The switching frequency is maintained at 50 kHz, and the switch, S is operated with a duty cycle, $\delta = 0.25$. The magnetizing inductance of the transformer, $L_m = 250 \mu\text{H}$ if seen from the side of the transformer which has N_1 turns. The turns ratio of the transformer (N_1/N_2) is 2. The output voltage of the converter is found to be 80 V. Find the load resistance, R_L . Assume the value of the capacitor, C is large, and hence ripple in the output voltage can be neglected.



Rubrics: No rubrics available.

 

CHAT

Roll No.: [22b3936]

Marks: 10.0

Question 5.

Part A: A single phase full bridge inverter circuit shown in Figure A is to be operated to produce a square wave output voltage, v_o at a frequency of $1/T$ Hz. Considering the load to be **capacitive** (i.e. when the load is fed by a sinusoidal source having a frequency of $1/T$ Hz, the load current leads the sinusoidal source voltage by a certain angle once steady state is reached). Plot the following waveforms for a period, T , when the circuit has attained steady state (i.e. once the dc component of the load current has become zero):

- Gating pulses for the switches S_1 to S_4 . (1 mark)
- Output voltage v_o across the load indicating its magnitude in terms of V_d . (1 mark)
- Approximate waveform of the output current, i_o . (1 mark)
- Mark on i_o that you have drawn in iii), the devices that are conducting at every instant over the period, T . (2 marks)

 


Figure A

 


Figure A

Part B: Now consider that the inverter of Figure B is feeding an R-L load. Plot (**along with the given waveforms of v_o**) the gating pulses for the switches S_1 to S_4 of the inverter (Figure A) if the output voltage waveform, v_o , to be obtained is:

i) as shown in Figure B. (3 marks)

ii) as shown in Figure C. (2 marks)

 


Figure B

 


Figure C

Rubrics: No rubrics available.



The three phase inverter shown in the Figure is to be operated as a square wave inverter such that the fundamental component of v_{BC} lags that of v_{AB} by 120° and fundamental component of v_{CA} lags that of v_{BC} by 120° while gating pulse for each device is provided for 180° . The input dc voltage for the inverter, V_d is 600 V (two dc voltage sources of magnitude 300 V each are connected in series having their connecting point at 'O').

a) Plot the gating pulses for the six switches, S_1 to S_6 along with v_{Ao} , v_{Bo} , v_{AB} , v_{An} when $Z_a = (10 + j0) \Omega$, $Z_b = (20 + j0) \Omega$, $Z_c = (20 + j0) \Omega$ and the switch, **MS is closed**. Comment on the presence/absence of third harmonic component in v_{AB} and v_{An} giving proper justification. (3 marks)

b) Plot the gating pulses for the six switches, S_1 to S_6 along with v_{Ao} , v_{Bo} , v_{AB} , v_{An} when $Z_a = (10 + j0) \Omega$, $Z_b = (20 + j0) \Omega$, $Z_c = (20 + j0) \Omega$ and the switch, **MS is open**. Comment on the presence/absence of third harmonic component in v_{AB} and v_{An} giving proper justification. (7 marks)

