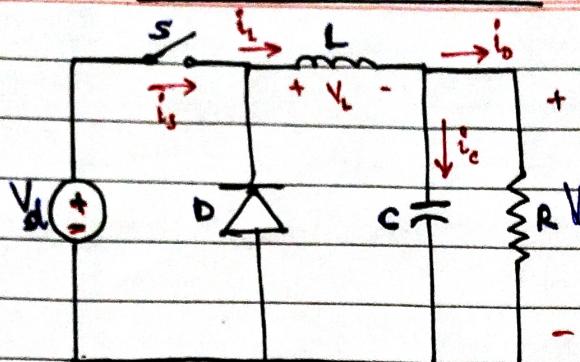


Buck Converter





In DCM,

@ Steady state:

$$I_0 = \bar{I}_L \Rightarrow \bar{I}_L = \frac{1}{2} (ST + \alpha T) \times (V_d - V_o) ST \times \frac{1}{T}$$
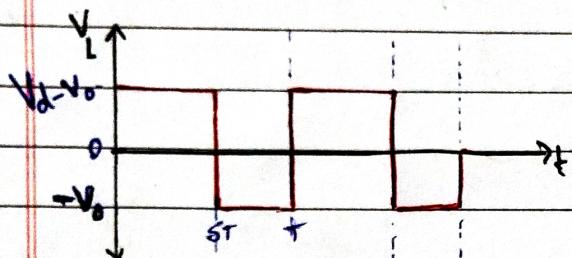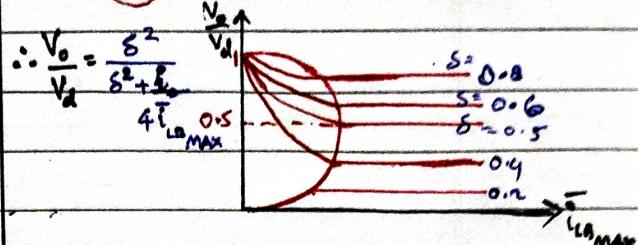
$$\Rightarrow I_0 = \frac{N_d T}{2L} \cdot S\alpha \Rightarrow \alpha = \frac{I_0}{4\bar{I}_{L_{\text{MAX}}}} S$$



$$N_d = 0 \Rightarrow (N_d - V_o) ST - V_o (1-S) T = 0$$

$$\Rightarrow M_o = \frac{V_o}{V_d} = S$$

DC voltage transfer fn


NOTE: If $i_L_{\text{peak}} = 2\bar{i}_L$, it is edge of CCM.

$$V_L = L \frac{di_L}{dt} \quad \therefore \bar{i}_L^{(\text{lim})} = i_L_{\text{peak}} / 2$$


$$\Rightarrow \bar{i}_{L_B} = \frac{1}{2} (V_d - V_o) \cdot ST \quad \text{where } V_d = V_o / 8$$

$$\bar{i}_{L_B} = \frac{V_d T \cdot S(1-S)}{2L}$$
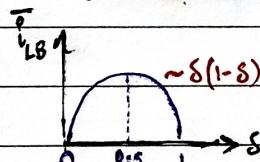
$$\bar{i}_{L_B}^{\text{MAX}} = \frac{V_d T}{8L}$$



$$\Delta V_o = \frac{T^2 (1-S)}{8LC}$$

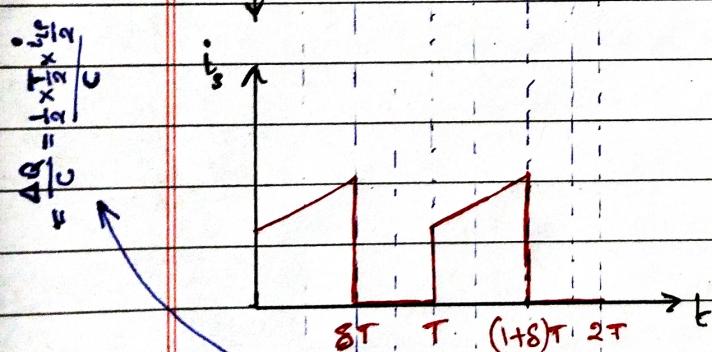

Upon reducing load... ($P_o: R_o \uparrow \Rightarrow I_0 \downarrow \Rightarrow \bar{i}_L \downarrow$)



But: \bar{i}_L does NOT change quickly
 $V_o = \frac{V_d}{R_o} \times \bar{i}_L$
 $\therefore (N_d - V_o) \rightarrow \text{less } -V_o \rightarrow \text{more rising slope falling slope}$ then eventually $\bar{i}_L \downarrow$

Continuous conduction mode
 Pulsed conduction mode

then eventually $\bar{i}_L \downarrow$

$\therefore V_o > V_{o_{\text{DCM}}}$

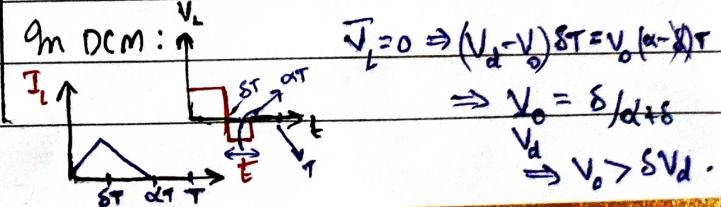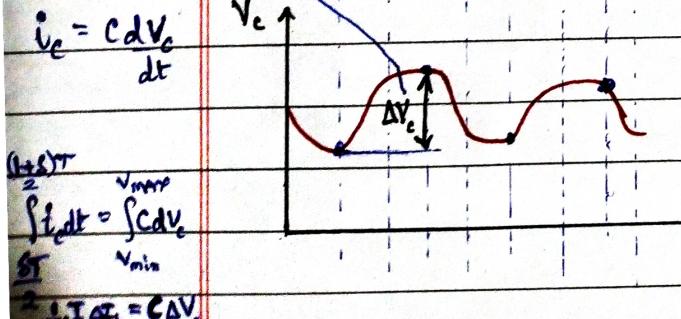NOTE: Steady state, $\bar{i}_L = I_0$ FOR CCM
 $\Rightarrow \frac{\Delta i_L}{2} = \frac{V_o}{R_o} \Rightarrow \frac{1}{2} (V_d - V_o) \cdot ST = \frac{V_o}{R_o} \cdot T$




$$\bar{i}_L = 0 \Rightarrow (V_d - V_o) ST = V_o (\alpha - 1) T$$

$$\Rightarrow V_o = \delta / (\alpha + \delta)$$


$$V_d \Rightarrow V_o > \delta V_d$$

Boost Converter

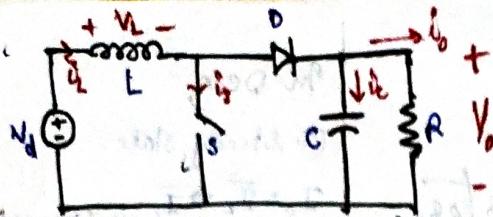

Date / /	/ /
Page No.	

Now, V_L

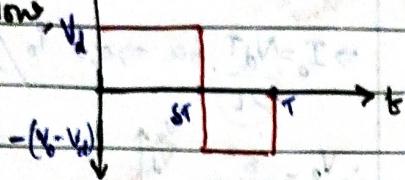

$$\bar{V}_L = 0 \Rightarrow V_d ST + (V_d - V_o)(1-s)T = 0$$

$$\therefore V_o/V_d = \frac{1}{1-s} \Rightarrow V_o > V_d .$$

* @ Steady state, voltage across $-t\tau$ should NOT change $\Rightarrow \bar{i}_c = 0 \Rightarrow \bar{i}_L = i_o$.


$$\therefore \text{again } I_o = V_d T s (1-s) \Rightarrow I_{o\text{MAX}} = \frac{V_d T}{s L}$$



If \bar{i}_L falls below threshold (in DCM):


$$V_d ST + (V_d - V_o)\alpha\tau = 0 \Rightarrow V_o = \frac{V_d}{1-\alpha}$$

$$\frac{V_o}{V_d} = \alpha$$

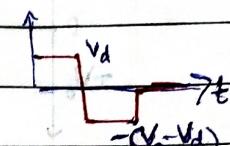


where α is again equal to
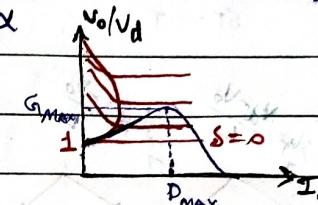
$$\boxed{\frac{i_o}{4I_{o\text{MAX}}} = \alpha}$$



Ripple: $\frac{\Delta V}{V_o} = C \Delta i_L \Rightarrow \Delta V = \frac{ST}{V_o RC} \Rightarrow \frac{\Delta V}{V_o} = \frac{s}{2f_s}$

Upon considering inductor resistance:

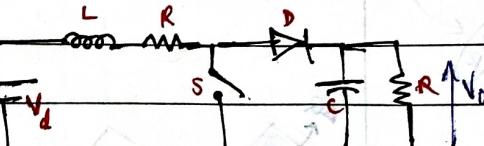


$$(V_d - i_L R_L) ST + (V_d - V_o - i_L R_L)(1-s)T = 0$$

Buck-Boost Converter

($i_L = 0$)

$$\boxed{G_{\text{MAX}} = \frac{1}{2}\sqrt{\frac{R}{R_L}}}$$
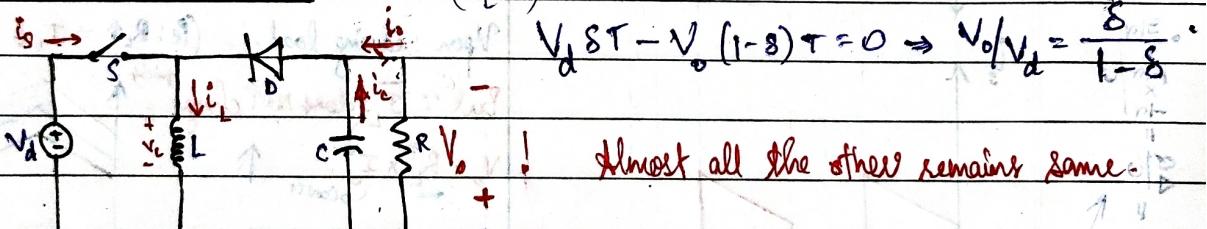
$$\boxed{D_{\text{MAX}} = 1 - \sqrt{\frac{R}{R_L}}}$$



$$V_d ST - V_o (1-s)T = 0 \Rightarrow V_o/V_d = \frac{s}{1-s}$$

! Almost all the other remains same.

* Buck-Boost converter inverts the polarity of the output w.r.t same $\frac{V_o}{V_d}$ as the ip.