
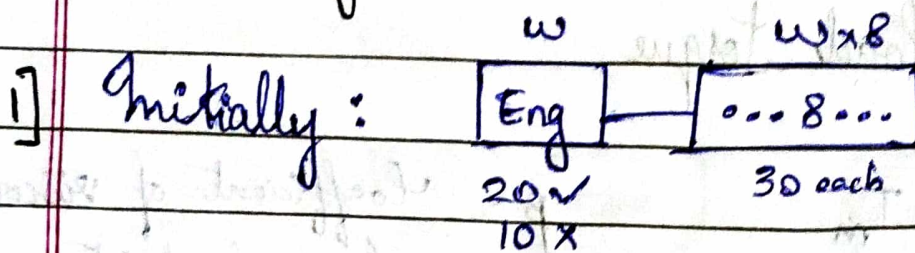


# Assignment - 1

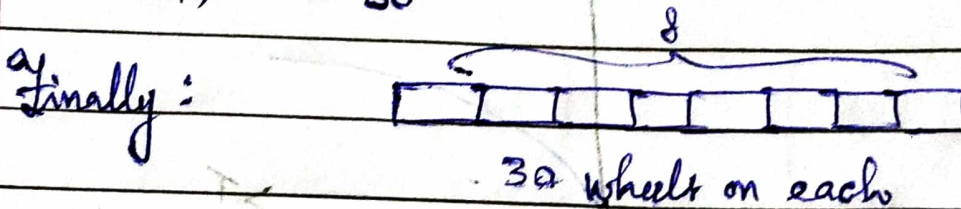

Here, maximum tractive effort of locomotive :

$$F_{E(\text{MAX})} = C_{\mu} \cdot \frac{w}{30} \times 20 \checkmark$$



Reqd MAX tractive effort =  $4 \times C_{\mu} \cdot \frac{w}{30} \times 20$

$$= \boxed{80} \times C_{\mu} \cdot \frac{w}{30}$$

⇒ We need 80 motorised wheels in total.

∴ There are 30 wheels for every coach of the suburban, and as there are 8 coaches,

$$\therefore \frac{80}{8} = \underline{\underline{10 \text{ motorised wheels per coach}}}$$


∴ Configuration :

80 motorized wheels (10 on each coach)  
160 dummy wheels (20 on each coach)




2]

SW-ON:

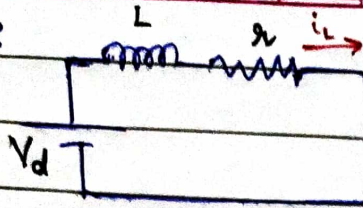

SW-OFF:

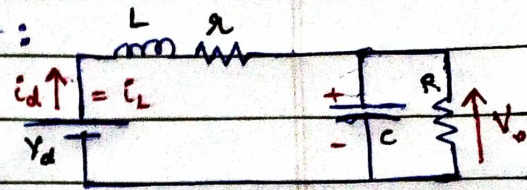

$$\overline{V_L} = 0 \Rightarrow (V_d - i_L r) \delta T + (V_d - V_o - i_L r) (1 - \delta) T = 0$$

$$\Rightarrow \cancel{V_d \delta} - \cancel{i_L r \delta} + V_d - V_o - i_L r - \delta V_d + V_o \delta + \cancel{i_L r \delta} = 0$$

Assumption:  $i_L \approx \overline{i_L} = \overline{i_d} = \overline{I_o} = \frac{V_o}{R} \times \frac{1}{(1-\delta)}$

$$\Rightarrow V_d = V_o - \delta V_o + \frac{V_o r}{R(1-\delta)} \Rightarrow \frac{V_o}{V_d} = \frac{1}{\frac{r}{R} + (1-\delta)} = \frac{1-\delta}{\frac{r}{R} + (1-\delta)^2}$$

B) for MAX of  $\frac{V_o}{V_d}$ , we require min of its denominator.

$\therefore$  using AM  $\geq$  GM on  $D_r$ :

$$\frac{\frac{r}{R(1-\delta)} + (1-\delta)}{2} \geq \sqrt{\frac{r}{R(1-\delta)} \times (1-\delta)}$$

$$\Rightarrow D_r|_{\min} = 2 \sqrt{\frac{r}{R}}$$

$$\Rightarrow \left. \frac{V_o}{V_d} \right|_{\max} = \frac{1}{2} \sqrt{\frac{R}{r}}$$

$\delta$  should be such that both terms are equal for AM = GM

$$\therefore \frac{r}{R(1-\delta)} = (1-\delta) \Rightarrow \delta = 1 - \sqrt{\frac{r}{R}}$$


$$A) \left. \frac{V_o}{V_d} \right|_{D=0} = \frac{1-0}{\frac{r}{R} + (1-0)^2} = \frac{R}{R+r}$$

$$\left. \frac{V_o}{V_d} \right|_{D=1} = 0$$



3]


1)

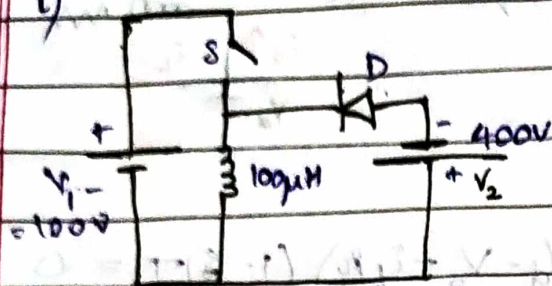

$\delta$  at boundary of CCM would be same as  $\delta$  at CCM  
 continuous  $\therefore$  using  $\overline{V_L} = 0$ ,

$$V_1 \delta T = V_2 (1 - \delta T)$$

$$\therefore \delta = 0.8$$

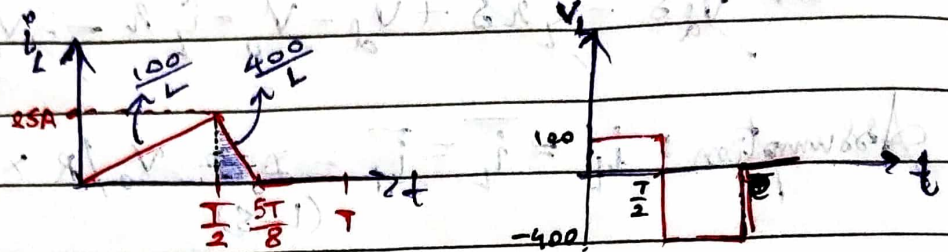2)  $D = 0.5$ :

Note that:

$$V_L = L \frac{di}{dt} \Rightarrow \int V_L dt = \int L di$$

$$\therefore \frac{100 \cdot T}{2} = i_{MAX} L$$

Now, the time in which this current dies out of the inductor =

$$\frac{400}{L} (time) = i_{MAX} \Rightarrow t = \frac{100 T}{L \cdot 2} \times \frac{L}{400} = \frac{T}{8} < \frac{T}{2}$$

$\therefore$  ckt is in DCM.

$\therefore$  Power transferred to  $V_2 = V_2 \cdot i_{avg}$  during action of  $V_2$

$$= V_2 \cdot \frac{\int i dt}{\int dt} = V_2 \left( \int_{T/2}^{5T/8} i dt + \int_{5T/8}^T 0 dt \right)$$

$$= 400 \cdot \left( \frac{1}{2} (T/8) \cdot \left( \frac{100 \cdot T}{L \cdot 2} \right) \right) = \frac{1250 T}{L}$$

$$= 1250 \times \frac{1}{20} \times 10^{-3} \times \frac{10^6}{100} = 625 W$$



c) @ Steady state,  $\Delta V_L = 0$   
 assuming CCM,


$$V_L = \begin{cases} 100V & (sT) \text{ --- ON} \\ -400 & (1-s)T \text{ --- OFF} \end{cases} \therefore 100sT + (-400)(1-s)T = 0 \Rightarrow s = 0.8$$

If  $s < 0.8 \rightarrow$  Discontinuous mode


If  $s > 0.8 \rightarrow$  Not steady state

If at all it can attain steady state with itself being in continuous mode, that would correspond to critical conduction mode.

4] i) a) ECM

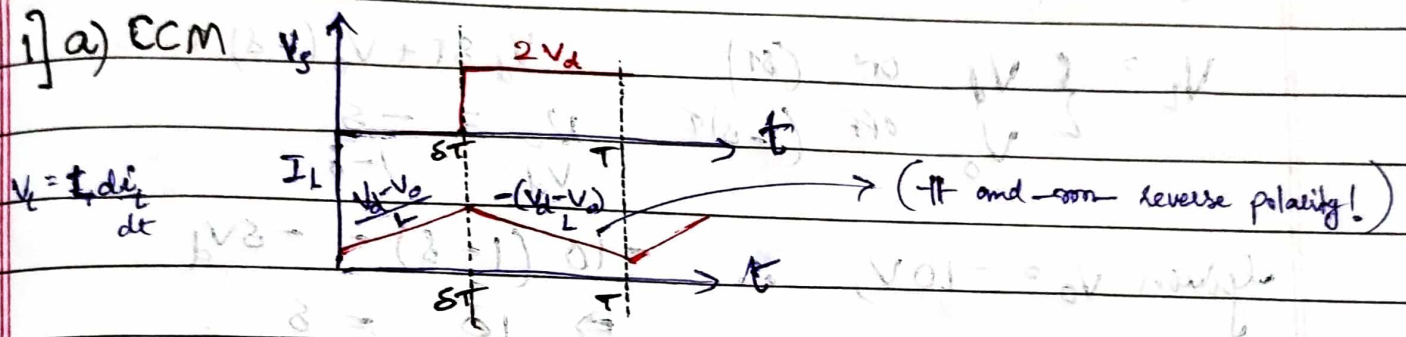

b) DCM

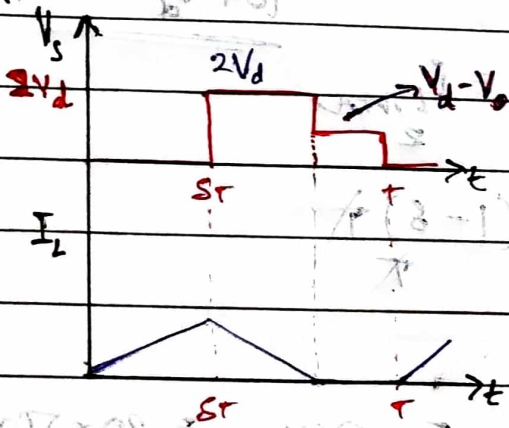

2] When SW is on, we will use  $\Delta V_L = 0$  to find  $V_o$ .

So,

When SW is on,  $V_L = V_d - V_o$

" " " OFF,  $V_L = -(V_d + V_o)$

$$\therefore (V_d - V_o) sT - (V_d + V_o) (1-s)T = 0 \Rightarrow \boxed{V_o = (2s-1)V_d}$$

$$3) i_{L_{pk-pk}} = \Delta i_L = i_{L_{MAX}} - i_{L_{min}}$$

$$P = (V_d - V_o) \delta T - (V_d - V_o) (1-\delta) T$$

$$= \frac{I}{L} \left[ \cancel{V_d \delta} - \cancel{V_o \delta} - V_d + V_o - \cancel{V_d \delta} + \cancel{V_o \delta} \right]$$

$$= \frac{2(\delta-1)V_d T}{L}$$

5) Given  $f_{sw} = 50 \text{ kHz} \Rightarrow T = 20 \mu s$

$$V_L = \begin{cases} V_d & \text{on } (\delta T) \\ V_o & \text{off } (1-\delta)T \end{cases}$$

$$V_d \delta T + V_o (1-\delta) T = 0$$

$$\frac{V_o}{V_d} = \frac{-\delta}{1-\delta}$$

Given  $V_o = -10V$ ,  $\therefore -10(1-\delta) = -5V_d$

$$\Rightarrow 10 = 5$$

$$i_o = -V_o/R_L, \quad i_o = \overline{i_L} = \frac{i_{L_{MAX}}}{2}$$

$$\Rightarrow \frac{-V_o}{R_L} = \frac{1}{2} \frac{V_d}{L} \times \delta T (1-\delta) T$$

$$\Rightarrow V_d = \frac{-2LV_o}{\delta T (1-\delta) T} = \frac{20L}{\delta T (1-\delta) T} = \frac{20 \times 50 \times 10^{-6}}{(1-\delta) T} (10+V_d)^2$$

$$0 = R \delta T (1-\delta) T \quad \delta (1-\delta) T \quad 20 \times 10^{-6} \times 10 \times V_d$$

$$\Rightarrow R_L V_d^2 = 5(10+V_d)^2 \Rightarrow V_d = \frac{\sqrt{5}(10+V_d)}{\sqrt{R_L}}$$

$$\Rightarrow V_d = \frac{10\sqrt{5}}{\sqrt{R_L - 5}}$$




$$i_d(pk) = \frac{V_d}{L} \delta T = \frac{V_d T}{L} \cdot \frac{10}{10+V_d} = \frac{V_d}{(10+V_d)} \cdot \frac{10 \times 20 \times 10^{-6}}{50 \times 10^{-6}}$$

$$= \frac{4V_d}{10+V_d} = \frac{40\sqrt{5}}{10\sqrt{5} - 10\sqrt{5} + 10\sqrt{5}} = \boxed{\frac{4\sqrt{5}}{\sqrt{5}}}$$

6]  $T = 200 \mu s$ ,  $D = 0.5$ ,  
 $L = 2.5 mH$ ,  $V_d = 100M$ ,  $V_o = 80V$

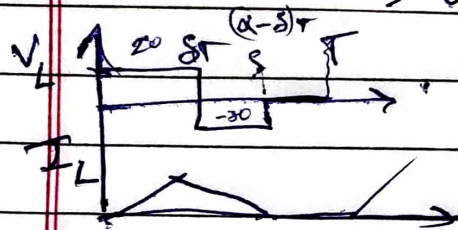Using  $V_L = 0$ ,  $(V_d - V_o) \delta T - V_o \alpha T = 0$   
 $\Rightarrow 20 \times 0.5 - 80\alpha = 0$   
 $\Rightarrow \alpha = 1/8$



$$i_{L(pk)} = \frac{V_d - V_o}{L} \times \delta T$$

$$= \frac{20}{2.5 \times 10^{-3}} \times \frac{0.2 \times 10^{-3}}{(T)} \times 0.5$$

$$= 0.8A$$

$$\therefore I_o = \overline{I_L} = \frac{1}{2} \times \cancel{i_{L(pk)}} \times \frac{(1 + \alpha)T}{T}$$

$$= \frac{0.8 \left( 0.5 + \frac{1}{8} \right)}{2} = 1/4$$

$$\therefore I_o = \frac{V_o}{R_L} = 0.25 \Rightarrow R_L = 4V_o = \boxed{320\Omega}$$