

Quiz-1.

Q1.

Equilibrium speed = $T = T_L$

$$\therefore 10 = 0.1 \omega_m \quad \text{or} \quad \omega_m = 100$$

(Steady state speed can be considered to be achieved when the speed is between 90 rad/s to 98 rad/sec.)

$$T = T_L + J \frac{d\omega_m}{dt} \quad \text{or} \quad \frac{d\omega_m}{dt} = \frac{T - T_L}{0.1}$$

2 marks

$$\text{or, } \frac{d\omega_m}{dt} = \frac{10 - 0.1 \omega_m}{0.1}$$

$$dt = \frac{d\omega_m}{100 - \omega_m} \quad \text{or} \quad t = \int_0^{95} \frac{d\omega_m}{100 - \omega_m}$$

1 mark.

Substituting $100 - \omega_m = z$, $-d\omega_m = dz$.

$$\text{when } \omega_m = 0, \quad z = 100$$

$$\omega_m = 95, \quad z = 5$$

$$\therefore - \int_{100}^5 \frac{dz}{z} = \int_5^{100} \frac{dz}{z} = [\ln(100) - \ln(5)]$$

$$= 2.99 \text{ sec} \approx 3 \text{ sec.}$$

2 marks

Full credit to be given if the steady state speed is considered to be any value lying between 90 rad/sec to 99 rad/sec.

If the final answer is written as 'infinity'
no credit (0 marks to be awarded) to be
given.

Q2. let the wt. of the locomotive = coach = W

For the locomotive driven train:

$$\text{Max}^m. \text{ T.E} = C_{\mu} \times \text{Wt. on the driving wheels} \quad N.$$

$$= C_{\mu} \times \frac{W}{20} \times 10 \quad N.$$

$$= C_{\mu} \frac{W}{2} \quad N. \quad (1 \text{ mark})$$

For the EMU


$$\text{Max}^m. \text{ T.E} = C_{\mu} \times \frac{12}{30} \times 3 \times W = \frac{36}{20} C_{\mu} W N$$

└ 3 marks.

$$\therefore \% \text{ increment in TE} = \frac{\frac{36}{20} - \frac{1}{2}}{\frac{1}{2}} \times 100 \%$$

$$= 260\%$$

└ 1 mark.

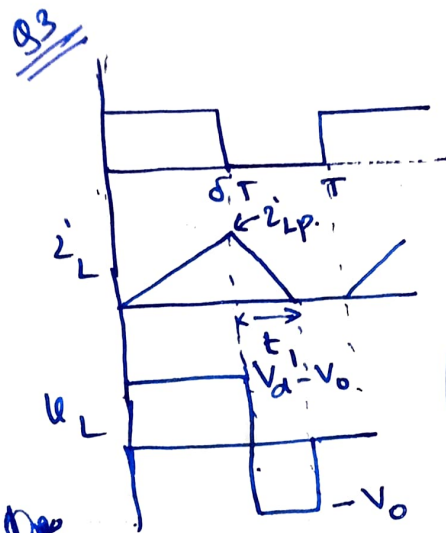

$$\dot{i}_{LP} = \frac{V_d - V_o}{L} \delta T$$

$$\dot{i}_{LP} - \frac{V_o}{L} t_1 = 0$$

$$\text{or, } \frac{V_o}{L} t_1 = \dot{i}_{LP}$$

$$\text{or } t_1 = \frac{\dot{i}_{LP} L}{V_o} = \frac{L}{V_o} \frac{V_d - V_o}{L} \delta T$$

$$= \frac{V_d - V_o}{V_o} \delta T$$

$$f_s = 5 \text{ KHz}, T = 0.2 \times 10^{-3} \text{ s} \quad (1 \text{ mark})$$

Let us assume the converter is operating in contⁿ mode. \therefore o/p voltage = $100 \times 0.5 = 50 \text{ V}$

$$\therefore \dot{i}_L = \dot{i}_o = \frac{50}{400} \approx 0.125 \text{ A}$$

the boundary current required for contⁿ mode of operation = $\frac{100 \times 0.2 \times 10^{-3}}{8 \times 2.5 \times 10^{-3}} = \frac{1}{10} \text{ A}$. Hence it is operating in discontinuous mode.

$$= \frac{100 - V_o}{V_o} \delta T$$

$$\dot{i}_L = \frac{1}{2} \times \left(0.5 T + \frac{100 - V_o}{V_o} 0.5 T \right) \times \frac{V_d - V_o}{L} 0.5 T \times \frac{1}{T} = \frac{V_o}{400}$$

$$\text{or, } \frac{1}{2} \times \frac{1}{2} \times \frac{1}{2} \left(T + \frac{100 - V_o}{V_o} T \right) \times \frac{100 - V_o}{L} = \frac{V_o}{400} \quad (3 \text{ marks})$$

$$\text{or, } \frac{1}{8} \left(1 + \frac{100 - V_o}{V_o} \right) T \times \frac{100 - V_o}{2.5 \times 10^{-3}} = \frac{V_o}{400}$$

$$\text{or, } \frac{1}{8} \left(\frac{100 + 100 - V_o}{V_o} \right) \frac{0.2 \times 10^{-3} \times (100 - V_o)}{2.5 \times 10^{-3}} = \frac{V_o}{400}$$

$$\text{or, } \frac{1}{8} \left(\frac{100}{V_o} \right) (100 - V_o) \frac{0.2}{2.5} = \frac{V_o}{400}$$

$$\text{or, } 100(100 - V_o) = \frac{V_o^2 \times 8 \times 2.5}{400 \times 0.2} = 0.25 V_o^2$$

$$\text{or } 0.25 V_o^2 = 100^2 - 100 V_o$$

$$\text{or } 0.25 V_o^2 + 100 V_o - 100^2 = 0$$

$$V_0 = \frac{-100 \pm \sqrt{100^2 + 4 \times 0.25 \times 100^2}}{0.5}$$

$$= \frac{-100 \pm \sqrt{10,000 + 10,000}}{0.5}$$

$$= \frac{-100 \pm 100\sqrt{2}}{0.5} = -200 \pm 200\sqrt{2}$$


Discarding the negative voltage

$$200(\sqrt{2} - 1) \text{ V} = 82.8 \text{ V}$$

1 mark.

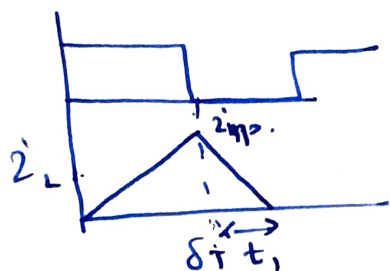Q4

$$T = \frac{1}{5 \times 10^3} \text{ s} = 0.2 \times 10^{-3} \text{ s.}$$



Assuming discontinuous conduction

$$i_{Lp} = \frac{100}{5 \times 10^3} \times 0.2 \times 0.2 \times 10^{-3}$$

$$= 0.8 \text{ A.}$$

$$0.8 - \frac{50}{5 \times 10^{-3}} t_1 = 0$$

$$\text{or, } t_1 = 0.08 \times 10^{-3} \text{ s}$$

3 marks


$$\therefore \bar{i}_L = \frac{1}{2} \times (0.08 + 0.2 \times 0.2) \times 10^{-3} \times 0.8 \times \frac{1}{0.2 \times 10^{-3}}$$

$$= \frac{1}{2} \times 0.12 \times \frac{0.8}{0.2} \text{ A} = 0.24 \text{ A.}$$

$$\therefore \text{the power transferred to } B_2 \text{ is } 50 \times 0.24 \text{ W} = 12 \text{ W.}$$

2 marks

2) The circuit will become uncontrollable once it starts operating in continuous mode of operation.

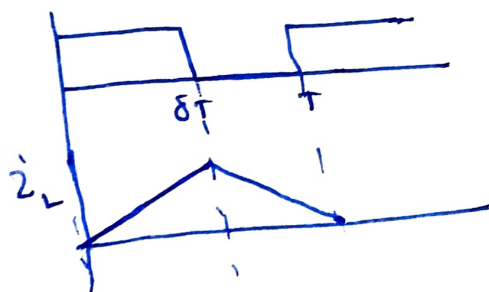At the boundary of contⁿ and discontⁿ mode of operation:

$$i_{Lp} = \frac{100}{L} \delta T$$

Further,

$$i_{Lp} - \frac{50}{L} (1-\delta) T = 0$$

5 marks

$$\text{or, } \frac{100}{L} \delta T - \frac{50(1-\delta)T}{L} = 0$$

$$\text{or, } 100\delta - 50 + 50\delta = 0$$

$$\text{or, } 150\delta = 50 \text{ or } \delta = \frac{1}{3} = 0.33$$

$$\therefore \delta_c = 0.33$$