


Endsem solution

navneet.com

Page No.:

Date: / /

3. Theory -

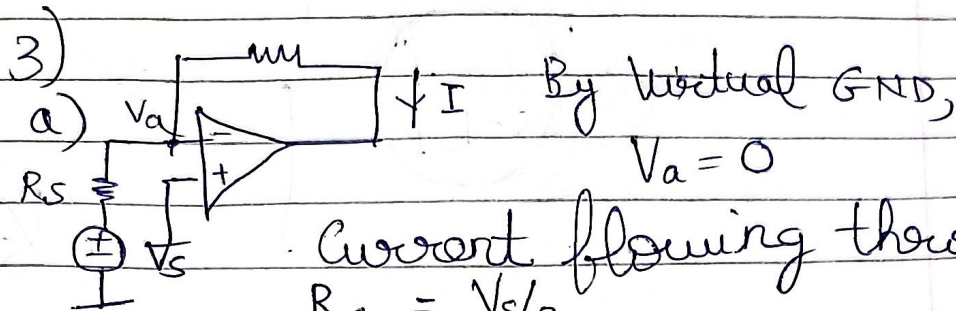


Current flowing through

$$R_s = V_s / R_s$$

→ Same current flows through R_L

$$\therefore I(R_L) = V_s / R_s \quad (1/2 M)$$

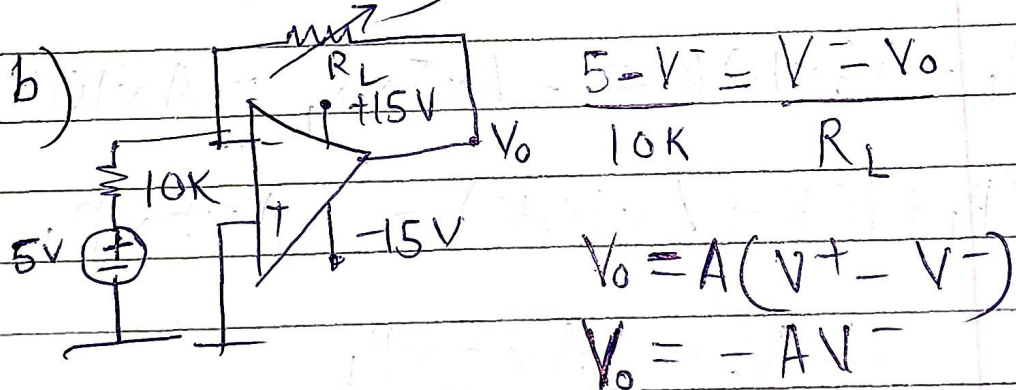→ Current through R_L does not change even if we change R_L (as long as OP-AMP does not saturate) $(1/2 M)$



$$5R_L - V^- R_L = 10K V^- - 10K V_o$$

$$\frac{5R_L + 10K \times V_o}{R_L + 10K} = V^-$$


$$\therefore V_o = -A \left(\frac{5R_L + 10K \times V_o}{R_L + 10K} \right)$$

$$V_o R_L + V_o \times 10K = -A \times 5 \times R_L - A \times 10K \times V_o$$

$$V_o (R_L + 10K + A \times 10K) = -A \times 5 \times R_L$$

$$\therefore V_o = \frac{-A \times 5 \times R_L}{R_L + 10K + A \times 10K}$$
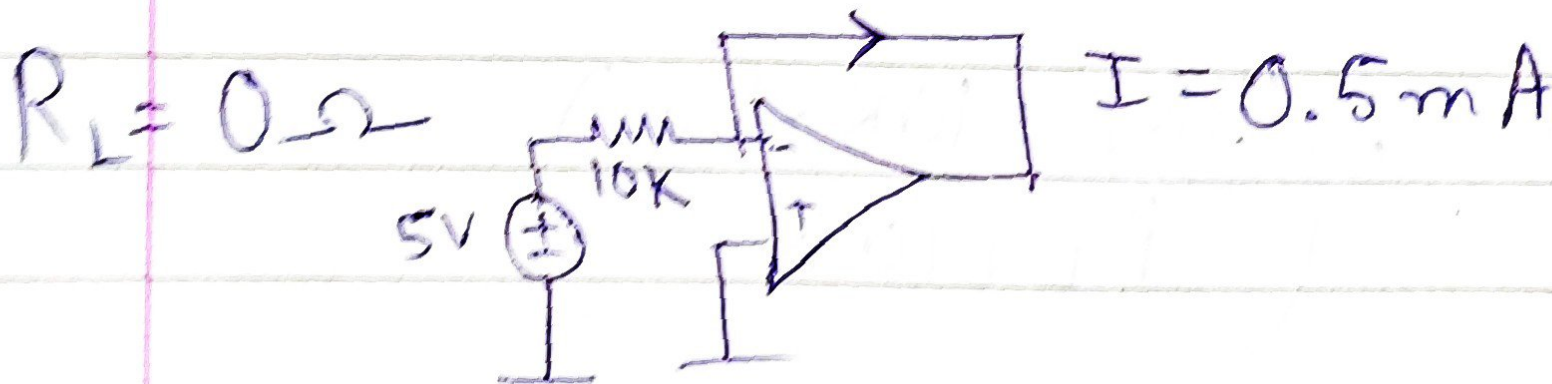
$$\therefore V_o = \frac{-5 R_L}{10K} \quad \left. \vphantom{\frac{-5 R_L}{10K}} \right\} \textcircled{\frac{1}{2} M}$$



$$V_0 = -15V, (a)$$

$$3 = \frac{R_L}{10K}$$


$$\therefore R_L = 30K$$

Page No.: 1/2
Date: 11/11

Given $R_L = 30K$, Current $I = 0.5mA$
After that OP-AMP \rightarrow sat

$$L \rightarrow R_L = 40K$$

$$V_0 = -15V$$

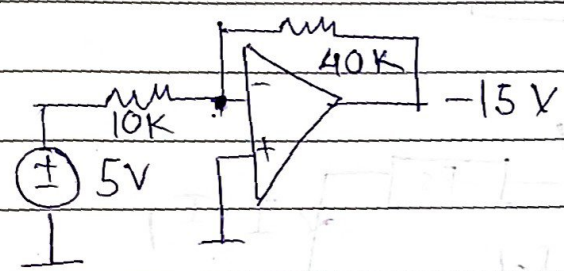

$$5 - V^- = \frac{V^- + 15}{4}$$

$$1 - \frac{V^-}{4} = \frac{V^- + 15}{4}$$

$$\therefore 20 - 4V^- = V^- + 15$$

$$\therefore 5 = 5V^-$$

$$\therefore V^- = 1V$$

$$I = 0.4mA$$

$$R_L = 50K$$

$$V_0 = -15V$$


$$5 - V^- = \frac{V^- + 15}{5}$$

$$25 - 5V^- = V^- + 15$$

$$10 = 6V^-$$


$$\therefore V^- = \frac{10}{6}$$

$$I = 0.33mA$$

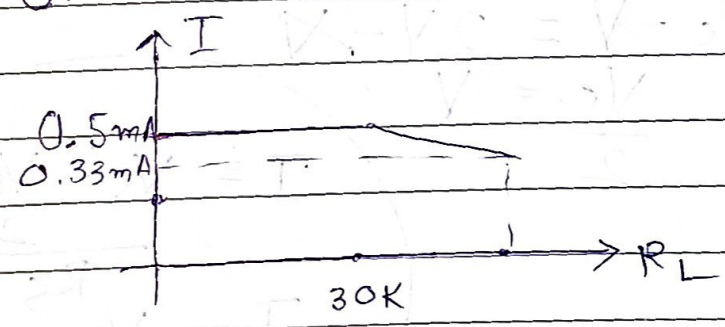

4. Hardware Implementation

1)

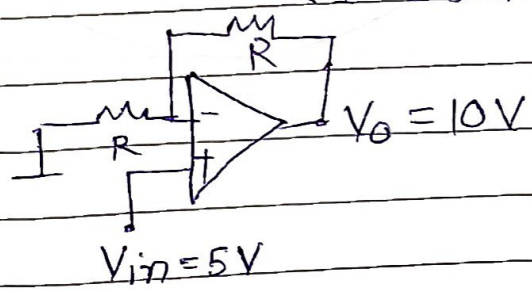

$$\frac{10 - 5}{R} \leq 0.5mA$$


$$\therefore \frac{5}{0.5} K\Omega < R$$

$$\therefore R > 10K\Omega$$

(2M)


2)

a)

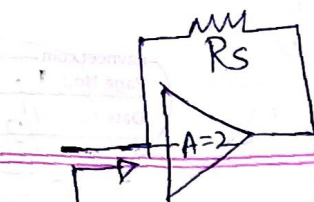


$$\frac{R_s}{1-A} = -R_s$$

$$R_s = 10\text{K}\Omega$$

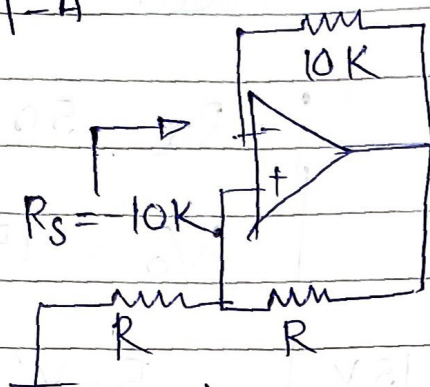

(1M)

b)

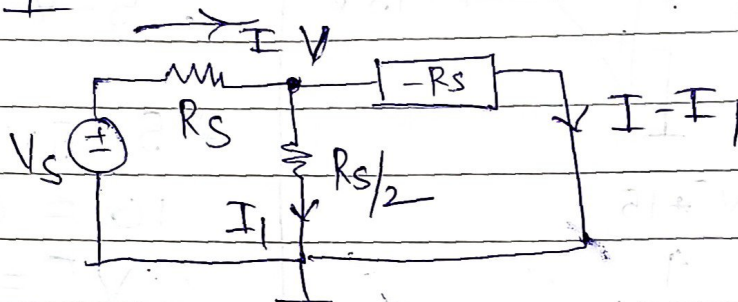

$$\frac{V_s - V}{R_s} = \frac{V}{R_s/2} + \frac{V}{-R_s} \quad (2M)$$

$$V_s - V = 2V - V$$


$$\frac{V_s}{2} = V$$

$$I = \frac{V_s - \frac{V_s}{2}}{R_s}$$

$$I = \frac{V_s}{2R_s}$$

3

3
(a)

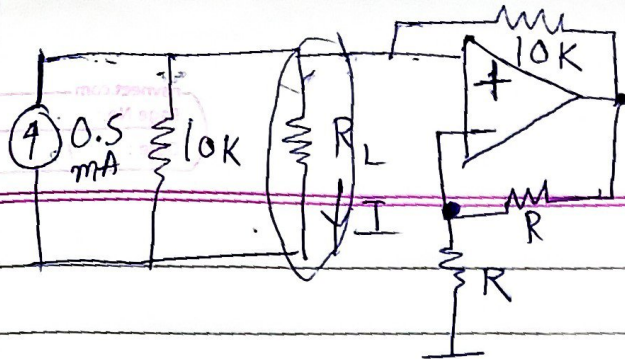


$$V_o = 15V$$

Page No.:

Date: / /

$$\leftarrow 10K \text{ } 0.75mA$$
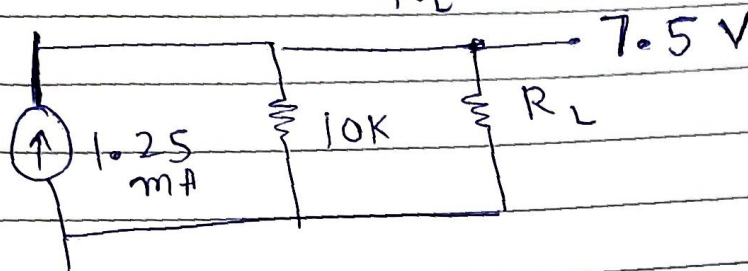
$$I_{\text{constant}} = \frac{V}{R_L} \text{ constant}$$



$$0.5 = \frac{10K}{10K + R_L} \times 1.25$$

$$5K + 0.5R_L = 12.5K$$

$$\therefore 0.5R_L = 7.5K$$

$$R_L \approx 15K$$

→ limiting value.

(3M)

4 → -ve R App

(a)

$$\frac{-R_s}{-R_s + R} \times V_{in} = V_{out} \rightarrow T.F.$$

$\left(\frac{1}{2} \right)^{1/2} M$

$$5 = \frac{-R_s}{-R_s + R}$$


$$-5R_s + 5R = -R_s$$

$$5R = 4R_s$$

$$R = \frac{4}{5}R_s$$

$$R = 8K\Omega$$

(1M)

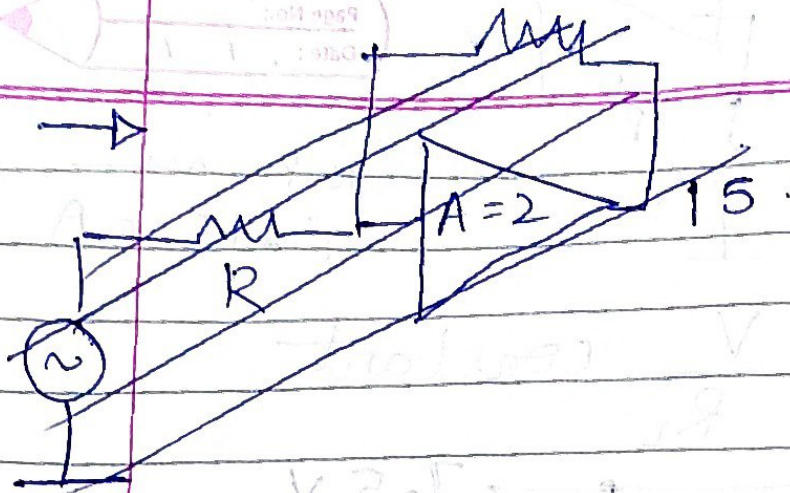

$$\left\{ \frac{-R_s}{-R_s + R} \right\} \times V_{in} = V_{out}$$

$$10 \times V_{in} = 15$$

$$\therefore V_{in} = 1.5 \text{ V}$$

$$\text{and } V_{in} = -1.5 \text{ V}$$

$$\text{Gain} = 11$$

$$V_{in} = 1.36 - (-1.36)$$